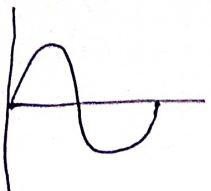


25/08/20


Digital Logic Design (86-8M)

84

Analog:



Digital

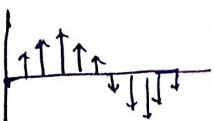

Advantages of Digital Compared to Analog

- * Effect of noise is less.
- * Digital is more efficient for data transmission.
- * When data storage is required then digital is best.
- * In digital data compression is possible.
- * In digital data can be encrypted. Hence data security is more.

Syllabus :

1. Binary System
2. Boolean Algebra
3. Logic gates
4. K-maps
5. Combinational Logic Circuits
6. Sequential logic circuits

1. Binary System

- (i) Number System - Conversions
- (ii) Binary Arithmetic
- (iii) Complements
- (iv) Binary Codes

Ref books:

1. Morris Mano (theory)
2. Anand Kumar (problems)

1. Binary System

Number system:

* Number systems are classified based on radix (r) or base.

∴ no. of symbols used

- (i) Decimal Number System ($r=10$) $\Rightarrow 0, 1, 2, \dots, 9$
- (ii) Binary Number System ($r=2$) $\Rightarrow 0, 1$
- (iii) Octal Number System ($r=8$) $\Rightarrow 0, 1, 2, \dots, 7$
- (iv) Hexadecimal Number System ($r=16$) $\Rightarrow 0, 1, 2, \dots, 9, A, B, C, D, E, F$

Note:

* Minimum digit of any number system is 0

* Maximum digit of any number system is $r-1$

Number System Conversion: for Integers

Decimal to Binary:

E: Convert given decimal number to binary

$$[46]_{10} = [?]_2$$

2	46
2	32-0
2	11-1
2	5-1
2	2-1
	1-0

$$= (101110)_2$$

Decimal to Octal

$$\text{Ex: } [567]_{10} = [?]_8$$

$$\begin{array}{r} 8 \mid 567 \\ 8 \quad | 70-7 \\ 8 \quad | 8-6 \\ \hline & 1-0 \end{array}$$

$$\therefore (567)_{10} = (1067)_8$$

Decimal to Hexadecimal:

$$\text{Ex: } [2766]_{10} = [?]$$

$$\begin{array}{r} 16 \mid 2766 \\ 16 \quad | 172-E \\ 16 \quad | A-C \\ \hline & \end{array}$$

$$\therefore (2766)_{10} = (\text{DDE})_{16} (\text{ACE})_{16}$$

Decimal to Any radix: If you want you to first minimize it.

$$\text{Ex: } (531)_{10} = (?)_7$$

$$\begin{array}{r} 7 \mid 531 \\ 7 \quad | 75-6 \\ 7 \quad | 10-5 \\ \hline & 1-3 \end{array}$$

$$\therefore (531)_{10} = (1365)_7$$

Number System Conversion for fractions:Decimal to binary

$$\text{Ex: } [0.25]_{10} = (?)_2$$

$$\text{i.e., } (0.25) = (0.01)_2$$

$$\begin{aligned} 0.25 \times 2 &= 0.5 \\ 0.5 \times 2 &= 1.0 \\ 0.0 \times 2 &= 0 \end{aligned}$$

↓ Stop with 0

$$\text{Eq: } (0.95)_{10} = (?)_2$$

$$\begin{array}{r}
 0.95 \times 2 = 1.9 \\
 0.9 \times 2 = 1.8 \\
 0.8 \times 2 = 1.6 \\
 0.6 \times 2 = 1.2 \\
 0.2 \times 2 = 0.4 \\
 0.4 \times 2 = 0.8 \\
 \rightarrow 0.8 \times 2 = 1.6
 \end{array}$$

$$\therefore (0.95)_{10} = (0.11\overline{10011001100}\dots)_2$$

Mixed

$$\text{Eq: } (95.75)_{10} = (?)_2$$

$$95.75 = 95 + 0.75$$

$$\begin{array}{r}
 95 \\
 \hline
 2 | 47 - 1 \\
 \hline
 2 | 23 - 1 \\
 \hline
 2 | 11 - 1 \\
 \hline
 2 | 5 - 1 \\
 \hline
 2 | 2 - 1 \\
 \hline
 1 - 0
 \end{array}$$

$$(95)_{10} = (101111)_2$$

$$\cancel{0.75} *$$

$$0.75 \times 2 = 1.5$$

$$0.5 \times 2 = 1.0$$

$$0.0 \times 2 = 0$$

$$(0.75)_{10} = (0.11)_2$$

$$\therefore \cancel{95} (95.75)_{10} = (101111.011)_2$$

Binary to Decimal:

$$(101110)_2 = (?)_{10}$$

$$1 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0$$

$$= 32 + 8 + 4 + 2$$

$$= (46)_{10}$$

- stop with 0

Q1: $(101111.11)_2 = (?)_{10}$

$$(2^8 + 2^5 + 2^4 + 2^3 + 2^2 + 2) + (2^{-1} + 2^{-2})$$

$$= 95 + \left(\frac{1}{2} + \frac{1}{4}\right)$$

$$= 95 + (0.75)$$

$$= (95.75)_{10}$$

Binary to Octal:

$$(10110011)_2 = (?)_8$$

$$\begin{array}{r} 010 \quad 110 \quad 011 \\ 2 \quad 6 \quad 3 \end{array}$$

$$\therefore (263)_8$$

$$(?) = (2F+2P)$$

$$2F \cdot 8 + 2P = 2F \cdot 8P$$

Octal to binary:

$$(513.241)_8 = (?)_2$$

$$\begin{array}{ccccccc} 5 & 1 & 3 & . & 2 & 4 & 1 \\ | & | & | & & | & | & | \\ 101 & 001 & 011 & & 010 & 100 & 001 \end{array}$$

$$\therefore (101001011 \dots 010100001)_2$$

2P	1
1 - fp	2
1 - 8C	3
1 - H	4
1 - Z	5
1 - S	6
0 - P	7

26/08/20

Q2

If

Hexadecimal to Binary: & Binary to Hexa Decimal.

Q2: $(101010.101001)_2 = (?)_{16}$

conversion of radix

$$\begin{array}{r} 0010 \quad 1010 \quad 1010 \quad 0100 \\ 0 \quad 1 \quad 0 \quad 1 \quad 0 \quad 1 \quad 0 \quad 0 \end{array}$$

$$\therefore (2A.A4)_{16}$$

$$0 \times 16^0 + 2 \times 16^1 + 8 \times 16^2 + 8 \times 16^3 + 10 \times 16^4 + 2 \times 16^5$$

Q3: $(5C3D.1F2)_{16}$

$$= (0101\ 1100\ 00111101 \cdot 0001\ 1111\ 0010)_2$$

Q3

Ans

(Q1) $(135)_2 + (114)_x = (323)_x$

Find x

$$(x^2 + 3x + 5) + (x^2 + ux + 4) = (3x^2 + 2x + 3)$$

$$\Rightarrow x^2 - 5x - 6 \geq 0$$

$$x^2 - 2x - 3x - 6 \geq 0$$

$$x(x-2) - (x-2)(x-3) \geq 0$$

$$x =$$

$$x^2 - 6x + x - 6 \geq 0$$

$$\Rightarrow (x+1)(x-6) \geq 0$$

$$x=6 \quad (\text{or}) \quad x=-1$$

never
↳ radix is not negative

$$\therefore x = 6$$

26/08/20

(Q2) If $(11x1y)_8 = (12c9)_{16}$, find x, y .

$$\underline{(001 \ 001 \ 001 \ \dots)}_2 = \underline{(0001 \ 0010 \ 1100 \ 1001)}_2$$

$$x = 101 = 5$$

$$\underline{(001 \ 001 \ \dots)}_2 = \underline{(0001 \ 0010 \ 1100 \ 1001)}_2$$

$$\therefore x = 011 = 3$$

$$y = 001 = 1$$

(Q3) Find no of 1's in the binary representation of below number.

$$(4 \times 4096) + (9 \times 256) + (7 \times 16) + 5$$

Sol:

$$= (4 \times 4096) + (9 \times 256) + (7 \times 16) + (5 \times 1)$$

$$= (4 \times 16^3) + (9 \times 16^2) + (7 \times 16) + (5 \times 1)$$

$$= [4975]_{16}$$

$$= (\underline{0100} \quad \underline{1001} \underline{0111} \underline{0101})_2$$

no of 1's = 8

- Q4 find no of 1's in binary representation of

$$3 \times 512 + 7 \times 64 + 8 \times 8 + 3$$

Sol:

$$= (3753)_8$$

$$= (011 \ 111 \ 101 \ 011)_2$$

\therefore no of 1's = 9

- Q5

- find the base or radix such that below equation holds

$$\frac{312}{20} = 13 \cdot 1$$

Sol:

let x be radix

Now converting into decimal

$$\frac{3x^2 + x + 2}{2x} = x + 3 + \frac{1}{x}$$

$$3x^2 + x + 2 = 2x \left(\frac{x^2 + 3x + 1}{x} \right) \quad (\because x \text{ can't be } 0)$$

$$3x^2 + x + 2 = 2x^2 + 6x + 2$$

$$x^2 - 5x = 0$$

$$\underline{\underline{x = 5}}$$

(Q6)

$$\sqrt{(224)_8} = (13)_8 \text{ find } r$$

Sol:

$$\sqrt{2r^2 + 2r + 4} = r + 3$$

S.O.B.O.S

$$2r^2 + 2r + 4 = r^2 + 6r + 9$$

$$\Rightarrow r^2 - 4r - 5 = 0$$

$$r^2 - 5r + r - 5 = 0$$

$$\underline{r=5} \quad r=-1$$

$$\therefore r=5$$

**

(Q7)

Consider $(123)_5 = (xy)_8$. Find no of possible solns for xy

Sol:

$$25 + (2 \times 5) + 3 = xy + 8$$

$$\Rightarrow xy = 30$$

WKT $x < y$ & xy must be ~~int~~ positive integers

$$\therefore x=1 \quad y=30$$

$$x=2 \quad y=15$$

$$x=3 \quad y=10$$

~~$x=5 \quad y=6$~~

Algo ~~y > 8~~~~Soln~~ solutions

∴ 3 solutions

(Q8)

$$(43)_x = (y3)_8 \text{ and find no of possible solns}$$

Sol:

$$4x + 3 = 8y + 3$$

$$\Rightarrow x = 2y$$

$$x=5 \Rightarrow y=2.5 \times$$

$$x=6 \Rightarrow y=3$$

$$x=8 \Rightarrow y=4$$

$$x=10 \Rightarrow y=5$$

$$x > 4$$

$$y < 8$$

$$x=12 \Rightarrow y=6$$

$$x=14 \Rightarrow y=7$$

∴ 5 Solutions

Binary Arithmetic

Binary addition

Eg: find $(1011)_2 + (1010)_2$

$$\begin{array}{r}
 & 1 & 0 & 1 & 1 \\
 \text{end carry} \leftarrow \textcircled{1} & 1 & 0 & 1 & 0 \\
 \hline
 & 1 & 0 & 1 & 0 & 1
 \end{array}$$

Eg: $(1111)_2 + (1110)_2$

$$\begin{array}{r}
 & 1 & 1 & 1 & 1 \\
 \textcircled{1} & 1 & 1 & 1 & 0 \\
 \hline
 & 1 & 1 & 1 & 0 & 1
 \end{array}$$

$\therefore (11101)_2$

Binary Subtraction:

Eg: $(1011)_2 - (1010)_2$

$$\begin{array}{r}
 1011 \\
 -1010 \\
 \hline
 0001
 \end{array}$$

Ans: $(0001)_2 = 1$

Eg: $(11011)_2 - (1100)_2$

$$\begin{array}{r}
 0 \overset{10}{\cancel{1}} \overset{10}{\cancel{0}} \overset{1}{\cancel{1}} \overset{1}{\cancel{1}} \\
 \times \cancel{x} \overset{10}{\cancel{0}} \overset{1}{\cancel{1}} \overset{1}{\cancel{1}} \\
 0 \overset{1}{\cancel{1}} \overset{1}{\cancel{0}} \overset{0}{\cancel{0}} \\
 \hline
 0 \overset{1}{\cancel{1}} \overset{1}{\cancel{1}} \overset{1}{\cancel{1}}
 \end{array}$$

~~Take borrow~~

the number taken as borrow is equal to radix -
i.e., $(10)_2$ in binary

Eg: $(11001)_2 - (1110)_2$

$$\begin{array}{r}
 0 \overset{10}{\cancel{0}} \overset{1}{\cancel{1}} \overset{10}{\cancel{0}} \overset{1}{\cancel{1}} \\
 \times \cancel{x} \overset{10}{\cancel{0}} \overset{1}{\cancel{1}} \overset{1}{\cancel{0}} \\
 0 \overset{1}{\cancel{1}} \overset{1}{\cancel{1}} \overset{0}{\cancel{0}} \\
 \hline
 0 \overset{1}{\cancel{1}} \overset{0}{\cancel{1}} \overset{1}{\cancel{1}}
 \end{array}$$

$\therefore (01011)_2$

$$\text{Q: } (1000001)_2 - (111110)_2$$

$$\begin{array}{r}
 & \overset{10}{\cancel{1}} \overset{10}{\cancel{1}} \overset{10}{\cancel{1}} \\
 1 & 0 & 0 & 0 & \cancel{1} & \cancel{1} & \cancel{1} \\
 & 0 & 1 & 1 & 1 & 1 & 0 \\
 \hline
 & 0 & 0 & 0 & 0 & 1 & 1
 \end{array}$$

$$\text{Eg: } (1010)_2 - (1011)_2$$

This is small - large

$$\begin{array}{r}
 1011 \\
 1010 \\
 \hline
 0001
 \end{array}$$

$$\therefore \text{Ans: } (-0001)_2$$

Octal Arithmetic

Octal addition:

$$\text{Eg: } (373)_8 + (264)_8$$

$$\begin{array}{r}
 3 7 3 \\
 2 6 4 \\
 \hline
 6 5 7
 \end{array}$$

$\therefore (373)_8 + (264)_8 = (657)_8$

$$\text{Eg: } \begin{array}{r} 1 \\ 4 5 7 \end{array}$$

$$\begin{array}{r} 5 6 4 \end{array}$$

$$\begin{array}{r} 1 2 4 3 \end{array}$$

$$\therefore (457)_8 + (564)_8 = (1243)_8$$

$$\text{Eg: } (345)_8 + (467)_8 = ?$$

$$\begin{array}{r}
 3 4 5 \\
 4 6 7 \\
 \hline
 1 0 3 4
 \end{array}$$

$$\therefore (1034)_8$$

number taken as
is equal to
 $(10)_2$ in binary

$$(167)_8 + (786)_8 = (278)_{10}$$

Find x, y, z

Sol:

1	1	1	1	0	1	1	0	1
2	6	7	8	9	8	7	6	5
$\underline{-}$								
y	x	z	6	5	4	5	6	7

Octal Subtraction

$$\begin{array}{r} \text{G: } (534)_8 - (365)_8 \\[1ex] \begin{array}{r} 4 \\ 5 \\ \hline 3 \end{array} \quad \begin{array}{r} 1^2 \\ 2 \\ 3 \\ \hline 4 \end{array} \quad \begin{array}{r} 14 \\ 4 \\ \hline 5 \end{array} \\[1ex] \hline \begin{array}{r} 1 \\ 4 \\ 7 \end{array} \end{array}$$

$$\therefore (534)_8 - (365)_8 = (147)_8$$

- Q10) which of the following represents $(E3)_{16}$
 a) $(CE)_{16} + (A2)_{16}$
 b) $(IBC)_{16} - (DE)_{16}$
 c) $(2BC)_{16} - (IDE)_{16}$
 d) $(200)_{16} - (11D)_{16} + (F2R)_{16}$

SOL:

$$\begin{array}{r} \text{a) } CE \\ \underline{A\ 2} \\ C \end{array} \quad \begin{array}{r} \text{b) } AC \\ 1\ B\ C \\ \underline{O\ D\ E} \\ 5 \end{array}$$

$$c) \begin{array}{r} \overset{A}{2} B C \\ \times \overset{B}{1} D E \\ \hline \text{E} Q \end{array} \quad d) \begin{array}{r} \overset{-1}{2} 0 0 \\ \times \overset{10}{1} 1 D \\ \hline \text{O} E 3 \end{array}$$

Complements

* complements are generally applied only on negative numbers.

Types of complements:

i) Diminished complement (or) 'r-1' complement

$$\text{formula: } r^n - r^{-m} - N$$

ii) Radix complement (or) r's complement

$$\text{formula: } r^n - N \quad \text{for } N \neq 0$$

and 0 for $N=0$

N is given number

r is radix

n is no of digits in integral part

m is no of digits in fractional part

Ex:

Complements in decimal system:

* diminished complement is 9's complement

* radix complement is 10's complement

27/08/20

9's complement:

Ex: Find 9's complement of $N = (632.54)_{10}$

$$r-1 \text{ complement} = r^n - r^{-m} - N$$

Here $r=10$, $n=3$, $m=2$, $N=632.54$

$$9\text{'s complement of } 10^3 - 10^{-2} - 632.54$$

$$= (367.45)_{10}$$

$\begin{array}{r} 10 \\ \times 10 \\ \hline 100 \\ + 10 \\ \hline 110 \\ \hline \end{array}$
 E 3

short cut to find q's complement:

* subtract each digit from 9

Ex: $N = 632 \cdot 54$

$$q's \text{ complement} = \underline{(367 \cdot 45)}_{10}$$

Note:

* To find any $r-1$ complement, subtract each digit of a given number from $r-1$ (including rightmost zeroes)

10's complement:

Ex: Find 10's complement for $N = [632 \cdot 54]_{10}$

$$\text{for } r's \text{ complement} = r^n - N$$

$$\text{i.e., } 10's \text{ complement} = 10^3 - 632 \cdot 54$$

$$= (367 \cdot 46)_{10}$$

shortcut to find 10's complement:

~~r's complement~~ =

$$10's \text{ complement} = q's \text{ complement} + 1$$

↳ (Add to LSB digit)

$$N = 632 \cdot 54$$

$$\begin{array}{r} q's \\ \longrightarrow 367 \cdot 45 \\ 10's \\ \longrightarrow \underline{+1} \\ \hline 367 \cdot 46 \end{array}$$

$$632 \cdot 54 + 1 = 633 \cdot 55$$

$$367 \cdot 45 + 1 = 368 \cdot 46$$

Shortcut 2:

→ Subtract the ^{1st} non-zero digit from 9. Also ~~make~~ keep remaining LSB '0' digits as '0's.

$$N = 632 \cdot 54$$

Ex:

$$10's \rightarrow (367 \cdot 46)_{10}$$

Ex: Find 10's complement of $(736.520)_{10}$

$$N = 736 \cdot 520$$

$$10's \rightarrow 263 \cdot 480$$

Note :-

* To find any r's complement, subtract the rightmost non-zero digit from r and & subtract remaining digits from r - 10's complement.
Also keep all the rightmost 0's (if exist) as '0' only.

**

* Ex: Find 9's & 10's complement of $(3024 \cdot 10500)_{10}$

Sol:

$$9's \text{ complement} \rightarrow (6975.80499)_{10}$$

$$10's \text{ complement} \rightarrow (6975.89500)_{10}$$

Binary Complements:1's complement:

Ex: find 1's complement of $(10101)_2$, given

10101

$$1's \rightarrow 01010$$

2's Complement

Eg: find 2's complement of $(10101)_2$

sol: In 2's complement, add 1 to 1's complement.

$$\begin{array}{cccc} 0 & 0 & 0 & 1 & 0 \\ & 1 & 0 & 1 & 0 \end{array}$$

$$2's \rightarrow (01011)_2$$

$$(345 + 632) \leftarrow$$

Eg: find 2's complement of $N = (1010 - 10100)_2$

$$\begin{array}{r} 1010 - 10100 \\ \hline \end{array}$$

$$2's \rightarrow 0101 - 01100$$

Eg: find 2's complement of $n = (1011 - 0101000)_2$

$$2's \rightarrow (0100 - 1011000)$$

Octal Complements: procedure is same as 2's complement but for octal numbers.

7's complement: (from 7) 2's complement with the first odd

Eg: find 7's complement of $(304 - 520)_8$

$$7's \rightarrow (473 - 257)_8$$

8's complement: (from 8) 2's complement with the first even

Eg: $n = (304, (567000)_8) \leftarrow$ from 8's complement

$$8's \rightarrow (473 - 271000)_8$$

2's complement giving

* similarly for 15's complement & 16's complement and any other complement, we follow the same procedure.

Signed Numbers

+ve number \rightarrow MSB = 0

-ve number \rightarrow MSB = 1

* Signed numbers can be represented in 3 ways:

(i) Signed magnitude method.

(ii) Signed 1's complement method.

(iii) Signed 2's complement method.

(i) Signed Magnitude method:

Eg: Represent +5, -5 in signed mag. method

5 \rightarrow 101 (unsigned representation)

+5 \rightarrow 0101 } signed representation
-5 \rightarrow 1101 }

Range: $-(2^{n-1}-1)$ to $(2^{n-1}-1)$

(ii) Signed 1's complement method:

Eg: Represent +5, -5 using 1's complement method

5 \rightarrow 101 (unsigned representation)
1101

+5 \rightarrow 0101 } signed representation

-5 \rightarrow 1010 }

Range: $-(2^{n-1}-1)$ to $(2^{n-1}-1)$

* Here -ve numbers are 1's complements of their positive counterparts.

Corresponding positive numbers.

(iii) Signed 2's complement method:

100

Eg: Represent +5, -5 in 2's complement

$$5 = 101$$

$$+5 = 0101$$

$$-5 = 1010$$

Range: (-2^{n-1}) to $(2^{n-1}-1)$

* Here -ve numbers are represented as 2's complements of their corresponding +ve numbers.

Eg: What is decimal equivalent of 1011 in 2's complement.

Sol:

Given

$$\begin{array}{r} 1011 \\ \text{noted for sign bit} \end{array}$$

$$\begin{array}{r} 1011 \\ \text{noted for sign bit} \end{array}$$

Here MSB is 1 ($\rightarrow 2^0$) of $(1-2^{n-1})$. \therefore it is -ve number

So this number is in complement form.

\rightarrow finding its 2's complement again will give the positive equivalent number

$$\begin{array}{r} 1011 \\ \text{noted 2's comp} \rightarrow 0100 \end{array}$$

$$\begin{array}{r} 0100 \\ \text{noted 2's comp} \rightarrow 0101 \end{array}$$

$$\begin{array}{r} 0101 \\ \text{noted 2's comp} \rightarrow 0110 \end{array}$$

* 2's complement representation allows sign extension.

$$\therefore (1011)_2 = (11011)_2 = (111011)_2$$

Q12 Minim

in

Q13 Let A

complement

Sol:

A =

- (Q1) To represent -17 , the minimum & maximum no. of bits required in 2's complement form is _____

Sol:

$$17 \rightarrow 10001$$

$$+17 \rightarrow 010001$$

$$-17 \rightarrow 101111$$

$$\therefore \text{min no of bits} = 6$$

Also ~~.....11110111~~

$$\therefore \text{max no of bits} = \infty$$

- (Q2) Minimum no of bits req to represent $(+32)_{10}$, ~~-32~~ $-(32)_{10}$

in 2's complement form is

Sol:

$$32 \rightarrow 100000$$

$$+32 \rightarrow 0100000$$

$$-32 \rightarrow \cancel{1000000}$$

~~1000000~~ \swarrow However leftmost '1' is not needed
(i.e., sign extension)

$$\therefore (1100000)_2 = (100000)_2 = -(32)_{10}$$

- (Q3) Let $A = 1111010$, $B = 00001010$ be two 8 bit 2's complement numbers. Their product in 2's complement form is.

Sol:

$$A = (1111010)_2 = (1010)_2$$

$$2's \rightarrow 0110$$

$$\therefore A = -6$$

$$B = (00001010)_2 = (01010)_2 \Rightarrow B = 10$$

$$A \times B = -60$$

$+60 \rightarrow 0111100$

$-60 \rightarrow 1000100$

In 8 bits $\rightarrow 11000100$ (\because sign extension)

28/08/20

- (Q14) The range of signed decimal numbers that can be represented by 6 bit 1's complement is _____

Sol:

$n=6$

$$\text{range: } -(2^{n-1}-1) \text{ to } (2^{n-1}-1)$$

$$\Rightarrow -(2^5-1) \text{ to } (2^5-1)$$

$$\Rightarrow -31 \text{ to } 31$$

Note:

→ Both 1's & 2's complement allow sign extension but sign magnitude method doesn't.

→ Signed magnitude & 1's complement has 2 representations for zero. But 2's complement has a unique representation.

(Q15)

Find 9's complement of $(36800)_9$

Sol: 9's complement

$$\begin{array}{r} ⑧ ⑨ \\ 36800 \\ \hline 52100 \end{array}$$


$$\therefore 52100$$

Note:

10's complement of $(000.00)_{10} = (000.00)_{10}$

Binary Codes

→ 2 types

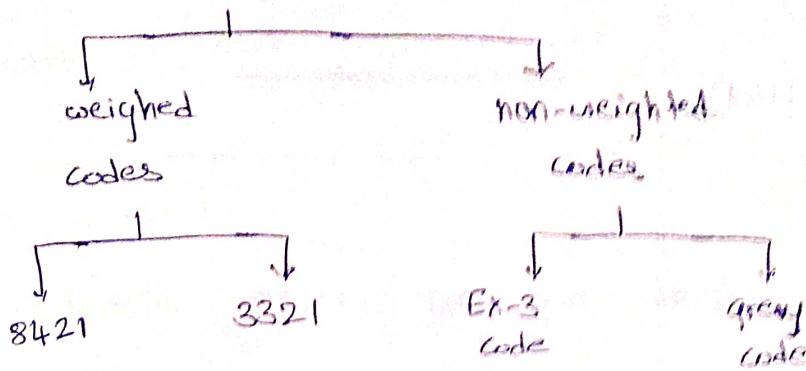

weighted Codes:

BCD code or 8421 code:

* BCD: Binary Coded Decimal

Decimal	BCD
0	0 0 0 0
1	0 0 0 1
2	0 0 1 0
3	0 0 1 1
4	0 1 0 0
5	0 1 0 1
6	0 1 1 0
7	0 1 1 1
8	1 0 0 0
9	1 0 0 1

Decimal	BCD
0	0 0 0 0
1	0 0 0 1
2	0 0 1 0
3	0 0 1 1
4	0 1 0 0
5	0 1 0 1
6	0 1 1 0
7	0 1 1 1
8	1 0 0 0
9	1 0 0 1

- BCD code is a 4-bit code.
- BCD code is sequential code (i.e., if add 1 in binary form of some decimal numbers gives the next number to it.)
- There are 6 invalid BCD codes. They are $\{1010, 1011, 1100, 1101, 1110, 1111\}$
- BCD & Binary are not equivalent.
- BCD is not a self complement code.

Eg: Represent $(93)_{10}$ in binary & BCD.

Sol:

Binary:

$$(1011101)_2$$

BCD:

$$\begin{array}{c} (93)_{10} \\ | \\ (1001 \ 0011)_{BCD} \end{array}$$

3321 Code

Decimal	3	3	2	1
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	1
5	1	0	1	0
6	1	1	0	0
7	1	1	0	1
8	1	1	1	0
9	1	1	1	1

logical complements
to each other

→ 3321

Non-weighted

Excess-3

* Here

→ For a decimal ~~number~~ digit, multiple ways may be possible to represent it under 3321. However we follow a unique a way for the purpose of making it easier.

We represent it such the

$$\text{Complement (4)} = 5$$

$$\text{Complement (3)} = 6$$

⋮

$$\text{Complement (0)} = 9$$

→ Hence we call this code as self complement code.

→ The
a's
know

Note: CS
To determine
code o

1
2
3
4
5
6
7
8
9

The code in which the codes of a digit and its 9's complement are logical complements to each other is known as self complement code.

Note: (short cut)

To determine whether any given weighted code is self complement code or not,

if sum of all weights = 9, ~~then~~ that code is self complement code (This is unidirectional)

→ 3321 is not a sequential code.

Non-weighted Codes:

Excess-3 Code:

* Here we add 0011 to the BCD (Not to binary)

Decimal	Ex-3 Code
0	0 0 11
1	0 1 00
2	0 1 01
3	0 1 10
4	0 1 11
5	1 0 00
6	1 0 01
7	1 0 10
8	1 0 11
9	1 1 00

BCD	X's 3 Code
→ 4-bit weighted code	→ 4 bit non-weight code
→ Sequential code	→ Sequential code
→ not a self-complement code	→ Self-complement code
→ 6 invalid BCD codes $\{1010, 1011, 1100, 1101, 1110, 1111\}$	→ 6 invalid codes $\{0000, 0001, 0010, 1101, 1110, 1111\}$

Gray

eg:


Gray code

→ gray code depends on modulo sum operator (\oplus)

Binary to Gray Code conversion

Ex:

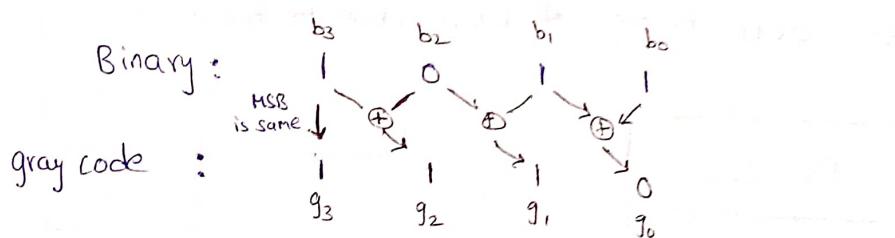Eg: Convert given binary number $(1011)_2$ into gray code



∴ gray code of $(1011)_2$ is (1110) gray

If $b_n b_{n-1} b_{n-2} \dots b_2 b_1 b_0$

If $b_{n-1} b_{n-2} b_{n-3} \dots b_2 b_1 b_0$ is a binary number, and let

$g_{n-1} g_{n-2} g_{n-3} \dots g_2 g_1 g_0$ be its gray code

then

$$g_{n-1} = g_{n-1}$$

$$g_{n-1} = b_{n-1}$$

$$g_i = g_{i+1} \oplus b_i, \quad i \neq n-1$$

Note:
From
In
One

Gray code to binary:

Eg: Convert given gray code (1110) to binary form

Gray code : binary form :

If $g_{n-1} g_{n-2} \dots g_1 g_0$ is a gray code and $b_{n-1} b_{n-2} \dots b_1 b_0$ be its binary form then

$$b_{n-1} = g_{n-1}$$

$$b_i = b_{i+1} \oplus g_i, \quad i \neq n-1$$

Eg: Express decimal numbers 0 to 7 in gray code using 3 bits

Decimal	binary	gray code
0	0 0 0	0 0 0
1	0 0 1	0 0 1
2	0 1 0	0 1 1
3	0 1 1	0 1 0
4	1 0 0	1 1 0
5	1 0 1	1 1 1
6	1 1 0	1 0 1
7	1 1 1	1 0 0

$$\begin{array}{r}
 & 0 8 \\
 & 0 1 \\
 \hline
 & 1 1 \\
 & 1 0
 \end{array}$$

Note :

From above example,

- In gray code any two consecutive number differ by exactly one bit. Hence gray code is called unit distance code.
 - It is also called as reflective code (\because practically it generated using mirror image)

29

→ It is also called as cyclic code. (\because 3-bit gray code is generated from 2-bit graycode, 4-bit gray code is generated from 3-bit graycode, ...))

ASCII Code

* 7-bit code

0 to 9	48 to 57
A to Z	65 to 90
a to z	97 to 122

Decimal	ASCII	Binary equivalent
0	48	0110000
1	49	0110001
2	50	0110010
3	51	0110011
4	52	0110100
5	53	0110101
6	54	0110110
7	55	0110111
8	56	0111000
9	57	0111001

Boolean Algebra

Laws:

* Commutative law:

$$A + B = B + A$$

$$AB = BA$$

* Associative law:

$$(A+B)+C = A+(B+C)$$

$$(AB)C = A(BC)$$

* Distributive law

$$A(B+C) = AB+AC$$

$$A+BC = (A+B)(A+C)$$

Rules or Postulates of Boolean algebra:

$$\rightarrow A + 0 = A$$

$$\rightarrow A + 1 = 1$$

$$\rightarrow A \cdot 0 = 0$$

$$\rightarrow A \cdot 1 = A$$

$$\rightarrow A \cdot A = A$$

$$\rightarrow A + \bar{A} = 1$$

$$\rightarrow A \cdot \bar{A} = 0$$

$$\rightarrow \overline{(A)} = A$$

$$\rightarrow A + AB = A \quad (A + AB = A(1+B) = A)$$

$$\rightarrow (A+B) \cdot (A+C) = A + BC$$

$$\rightarrow A + \bar{A}B = A + B$$

Simplify the following boolean functions

$$^*(i) f(A, B, C) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C$$

$$= \bar{A}\bar{C}(\bar{B}+\bar{B}) + \bar{A}\bar{B}C = \bar{A}\bar{C} + \bar{A}\bar{B}C$$

$$= \bar{A}(BC + \bar{C}) = \bar{A}(\bar{C} + B) = \bar{A}(B + \bar{C})$$

Variables: A, B, C, ...

116

Complements: $\bar{A}, \bar{B}, \bar{C}, \dots$

Literals: $A, \bar{A}, B, \bar{B}, \dots$

→ we need to minimize until we get min no. of literals

Ex for example

$\bar{A}(B+C)$ has 3 literals

$$\text{Eq} : (b\bar{c} + \bar{a}\bar{d})(a\bar{b} + c\bar{d})$$

sol:

$$b\bar{c}a\bar{b} + b\bar{c}c\bar{d} + \bar{a}\bar{d}a\bar{b} + \bar{a}\bar{d}c\bar{d}$$

$$0 + 0 + 0 + 0$$

$$= 0$$

Eq: simplify

$$f = (A + \bar{B})(\bar{A} + \bar{B} + D)(\bar{B} + C + \bar{D})$$

$$= (0 + A\bar{B} + AD + \bar{A}\bar{B} + \bar{B} + \bar{B}D)(\bar{B} + C + \bar{D})$$

$$= \underline{A\bar{B} + A\bar{B}C + A\bar{B}\bar{D}} + \underline{A\bar{B}D + ACD + 0} + \underline{\bar{A}\bar{B} + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{D}}$$

$$+ \bar{B} + \bar{B}C + \bar{B}\bar{D} + \bar{B}D + \bar{B}CD + 0$$

$$= A\bar{B} + A\bar{B} + ACD + \bar{A}\bar{B} + \bar{B}$$

$$= \underline{A\bar{B} + \bar{A}\bar{B} + \bar{B} + ACD}$$

$$= \bar{B} + ACD$$

∴ 4 literals

Duality Theorem:

$$\ast 0 \leftrightarrow 1, \quad \ast \leftrightarrow +$$

Eg: apply duality to the following function

$$f = A[\bar{B} + C]$$

~~$f = A[\bar{B} + C]$~~

$$f_D = (A) + (\bar{B} \cdot C)$$

Note: while applying duality, variables remain same.

Eg: Apply duality for $f = A + 1$

$$f_D = A \cdot 0$$

$$f_D = \bar{B} + 1 = 1$$

$$\Rightarrow \bar{B} \cdot 0 = 0$$

Eg: Find duality then simplify

$$f = AB + BC + CA$$

$$\Rightarrow f_D = (A + \bar{B})(\bar{B} + C)(C + A)$$

$$f_D = (B + \bar{A})(C + A)$$

$$f_D = BC + BA + AC + AC$$

$$f_D = AB + BC + CA$$

$$\text{Here } f_D = f$$

Such function is called self dual function

Self Dual Function:

A function f is called as self dual function, if $f_D = f$

A function is self dual
 \Rightarrow exactly one element
 of every complementary pair is present

If $i \in m$ & then
 $2^n - 1 - i \in M$
 such function is called
 self dual

(Q14) By using 2-variables, no of possible boolean functions is _____

Sol :

A	B	F
0	0	0/1 → 2 ways
0	1	0/1 → 2 ways
1	0	0/1 → 2 ways
1	1	0/1 → 2 ways

$$\text{i.e., } 2^4 \text{ ways} = 16$$

$$(A+B)(A+B)(A+B)(A+B)$$

(Q15) By using 2-variables, no of possible self dual functions is _____

Sol :

$f = A, f = \bar{A}, f = B, f = \bar{B}$
are self dual functions

$$\therefore 4$$

(Q16) By using 2-variables, no of possible self dual functions is _____

Sol:

Note:

→ Using n variables, no of function possible = $\frac{1}{2}(2^n)$

→ Using n variables, no of self dual functions possible = $\frac{1}{2}(2^{n-1})$

Demorgan's theorem:

$$\rightarrow \overline{A+B} = \overline{A} \cdot \overline{B}$$

$$\text{Sily } \overline{A+B+C+\dots} = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \dots$$

$$\rightarrow \overline{A \cdot B} = \overline{A} + \overline{B}$$

$$\overline{A \cdot B \cdot C \cdot D \dots} = \overline{A} + \overline{B} + \overline{C} + \overline{D} + \dots$$

Ex: Simplify

$$f = \overline{ABC} \cdot D$$

Sol:

$$\text{given } \overline{((\overline{AB})C)D}$$

$$f = \overline{(\overline{AB}C)} + \overline{D}$$

$$= (\overline{AB})C + \overline{D}$$

$$= (\overline{A} + \overline{B})C + \overline{D}$$

31/08/20

(Q16)

simplify

$$f = \underbrace{B + AD + BC}_{+} + \overline{B + A(C+D)}$$

$$f = B + AD + \overline{B} \cdot \overline{A(C+D)}$$

$$(f = B + AD + \overline{B} \cdot (\overline{A} + \overline{C} \overline{D}))$$

$$f = B + AD + \overline{A} \overline{B} + \overline{B} \overline{C} \overline{D}$$

$$f = \underbrace{B + \overline{A} \overline{B}}_{+} + AD + \overline{B} \overline{C} \overline{D}$$

$$f = (B + \overline{A}) + AD + \overline{B} \overline{C} \overline{D}$$

$$f = B + (\overline{A} + AD) + \overline{B} \overline{C} \overline{D}$$

$$f = B + \overline{A} + \underbrace{AD}_{+} + \overline{B} \overline{C} \overline{D}$$

$$f = B + \overline{A} + D + \overline{B} \overline{C}$$

$$f = (B + \overline{B} \overline{C}) + \overline{A} + D$$

$$f = B + \overline{C} + \overline{A} + D$$

$$f = \overline{A} + B + \overline{C} + D$$

Method 2:

$$f = B + AD + BC + \overline{B + A(C+D)}$$

$$= (B + AD) + (B + AD) + AC$$

$$= (B + AD) + \overline{(B + AD)} \cdot \overline{AC}$$

$$= (B + AD) + \overline{AC} = B + AD + \overline{A} + \overline{C} = B + \overline{A} + D + \overline{C}$$

$$= \overline{A} + B + \overline{C} + D$$

Complement of a Boolean function:

114

Eg: find complement of the given boolean function

$$f = \bar{x}y\bar{z} + \bar{x}yz$$

Sol:

$$\begin{aligned}\bar{f} &= \overline{(\bar{x}y\bar{z} + \bar{x}yz)} \\ &= (\bar{\bar{x}}y\bar{\bar{z}}) \cdot (\bar{\bar{x}}y\bar{z}) \\ &= (x + \bar{y} + z)(x + \bar{y} + \bar{z})\end{aligned}$$

Eg: The simplified form of the following

$$f = (A\bar{B}\bar{C} + C\bar{D}) + ((\bar{A} + B + C)(\bar{C} + D))$$

$$f = \cancel{A\bar{B}\bar{C}} + \cancel{C\bar{D}} + (\bar{A}\bar{C} + \bar{A}D + \cancel{B\bar{C}} + BD + \cancel{CD})$$

$$f = C + \bar{C}(A\bar{B} + \bar{A} + B) + \bar{A}D + BD$$

$$f = C + \bar{C}(\bar{A} + \bar{B} + B) + \bar{A}D + BD$$

$$f = C + \bar{C}\bar{A} + \bar{A}D + BD$$

$$f = C + \bar{A} + \bar{A}D + BD$$

$$f = C + \bar{A} + BD$$

(Q17) Simplify $f = (A\bar{B}\bar{C} + C\bar{D}) + [(\bar{A} + B + C)(\bar{C} + D)]$


Sol:

$$\text{let } x = A\bar{B}\bar{C} + C\bar{D}$$

$$\bar{x} = \overline{A\bar{B}\bar{C} + C\bar{D}} = (\bar{A} + B + C)(\bar{C} + D)$$

$$\text{now } f = x + \bar{x} = 1$$

Boolean function forms

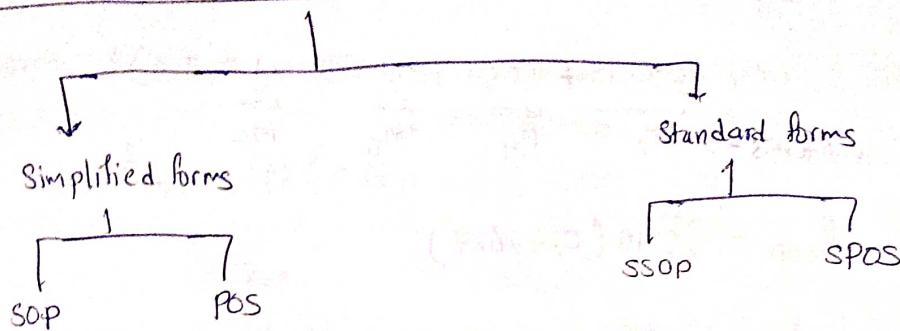

SOP (Sum of Products):

$$f_{SOP} = \underbrace{\bar{B}\bar{C} + AB}_{2 \text{ terms}}$$

In the terms we have operator '+' (sum)

How the literal we have operator '•' (product)

SSOP: (Standard sum of Product)

$$f_{SOP}(A, B, C) = \bar{B}\bar{C} + AB$$

SSOP is SOP in which every term must have all variables' literals

$$\bar{B}\bar{C} + AB$$

$$(1)(\bar{B}\bar{C}) + (1)(AB)$$

$$(A + \bar{A})(\bar{B}\bar{C}) + (AB)(C + \bar{C})$$

$$f_{SSOP} = A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + AB\bar{C} + ABC$$

→ Each term in SSOP is called as minterm

It is indicated with "m".

~~$f_{SSOP} = A$~~

Eg: Let $f_{ssop} = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + AB\bar{C} + ABC$

i.e., $\underbrace{000}_{M_0} + \underbrace{100}_{M_4} + \underbrace{110}_{M_6} + \underbrace{111}_{M_7}$
minterms $\rightarrow M_0, M_4, M_6, M_7$

$$\therefore f_{ssop} = \sum m(0, 4, 6, 7)$$

POS: (Product of Sum)

Eg: $f_{pos} = (x+y) \cdot (\bar{y}+z)$

terms are separated by product
within a term, literals are separated by sum

SPOS: (Standard Product of sum)

Ques: Convert $f_{pos} = (x+y) \cdot (\bar{y}+z)$ into SPOS

$$f_{pos}(x, y, z) = (x+y)(\bar{y}+z)$$

$$= (x+y+0)(0+\bar{y}+z)$$

$$= (x+y+z \cdot \bar{z})(x\bar{x}+\bar{y}+z)$$

$$f_{spos} = (x+y+z)(x+y+\bar{z})(x+\bar{y}+z)(\bar{x}+\bar{y}+z)$$

In SPOS each term is called maxterm.

Maxterm is indicated using "M"

$$f_{spos} = (x+y+z)(x+y+\bar{z})(x+\bar{y}+z)(\bar{x}+\bar{y}+z)$$

Maxterm $\underbrace{000}_{M_0} \underbrace{001}_{M_1} \underbrace{010}_{M_2} \underbrace{110}_{M_6}$
Maxterms $\rightarrow M_0, M_1, M_2, M_6$

$$\therefore f_{spos} = \prod M(0, 1, 2, 6)$$

16

Conversion
Eg: Conv

(18) Let

(19) Simplifying

9

Conversions blw . canonical form

Eg: convert $f(A, B, C) = \sum m(1, 3, 6)$ into SPOS
 \downarrow absent terms (0 to 7)

$$f_{SPOS} = \prod M(0, 2, 4, 5, 7)$$

~~Ans~~

$$= (A + B + C)(A + \bar{B} + C)(\bar{A} + B + C)(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + \bar{C})$$

(Q18) Let $\otimes *$ be defined as

$$x * y = \bar{x} + y \quad \text{let } z = x * y$$

value of $z * x$ is

Sol:

$$\begin{aligned} (\bar{x} * y) * x &= ((\bar{x} + y)) * x \\ &\approx xy \end{aligned}$$

$$z * x = \bar{z} + x$$

$$\begin{aligned} &= (\bar{\bar{x}} + y) + x = x\bar{y} + x \\ &= x \end{aligned}$$

(Q19) Simplified SOP form of $(P + \bar{Q} + \bar{R})(P + \bar{Q} + R)(P + Q + \bar{R})$

Sol:

$$\text{given } f = \prod M(3, 2, 1)$$

$$= \sum m(0, 4, 5, 6, 7)$$

$$= \underline{\bar{P}\bar{Q}\bar{R}} + \underline{P\bar{Q}\bar{R}} + \underline{P\bar{Q}R} + \underline{PQR} + \underline{PQR}$$

$$= \underbrace{\bar{Q}\bar{R} + P\bar{Q}R + PQ}_{8}$$

$$= \bar{P}\bar{Q}\bar{R} + P$$

$$= P + \bar{Q}\bar{R}$$

(Q20)

If $x=1$ in the logic equation

$$\left[x + z \{ \bar{y} + (\bar{z} + x\bar{y}) \} \right] \{ \bar{x} + \bar{z}(x+y) \} = 1$$

then

- a) $y=z$ b) $y=\bar{z}$ c) $z=1$ d) $z=0$

Sol:

$$x=1 \Rightarrow$$

$$\left[z \{ \bar{y} + (\bar{z} + \bar{y}) \} \right] \cdot ($$

$$(1) \{ 0 + \bar{z}(1+y) \} = 1$$

$$\bar{z}y = 1 \quad \bar{z} = 1$$

$$\Rightarrow z=0 \quad y=1 \quad \Rightarrow z=0$$

(Q21)

Simplify $(x+y)(x+\bar{y}) + \overline{(x\bar{y}) + \bar{x}}$

Sol:

$$(x+y\bar{y}) + \overline{x\bar{y}} \cdot x$$

$$x + (\bar{x}+y) \cdot x$$

$$x + x\bar{x} + xy = x + xy = x$$

(Q22)

The boolean expression $xy + (\bar{x}+\bar{y})z$ is equivalent to

- a) $xy\bar{z} + \bar{x}\bar{y}z$ b) $\bar{x}\bar{y}\bar{z} + xyz$
 c) $(x+z)(y+z)$ d) none

Sol:

$$xy + (\bar{x}+\bar{y})z = \cancel{xy} + \cancel{xz} + \cancel{yz}$$

$$\text{let } xy = p \Rightarrow \bar{p} = \bar{x} + \bar{y}$$

$$\therefore xy + (\bar{x}+\bar{y})z = p + \bar{p}z = p + z$$

$$= xy + z$$

01/09/20

Logic Gates:


Basic gates

(i) NOT (ii) AND (iii) OR


(iv) NAND (v) NOR

(vi) Ex-OR (vii) Ex-NOR


i) NOT gate (inverter):

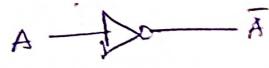

ii) AND Gate:

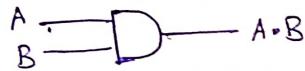

iii) OR Gate:

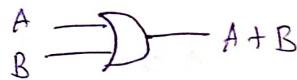

iv) Note:

→ AND, OR, NOT are called basic gates or AOI gates

AND OR INVERTER


iv) NAND gate:



v) NOR gate:



vi) Ex-OR: (Exclusive OR) (XOR)

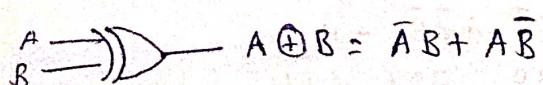

2) Ex-NOR (XNOR) :

$$\begin{array}{c} A \\ B \end{array} \Rightarrow \text{D} \quad A \oplus B = \overline{AB} + AB$$

Properties of XOR logic gate

$$\rightarrow A \oplus B = A\bar{B} + \bar{A}B$$

$$\rightarrow A \oplus 0 = A$$

$$\rightarrow A \oplus 1 = \bar{A}$$

$$\rightarrow A \oplus A = 0$$

$$\rightarrow A \oplus \bar{A} = 1$$

Consider

$$\begin{aligned} \cancel{\text{AEP}} \\ \overline{A \oplus B} &= \overline{\overline{AB} + AB} \\ &= (\bar{A} + B)(A + \bar{B}) \\ &= \bar{A}A + \bar{A}\bar{B} + AB + B\bar{B} \\ &= \bar{A}\bar{B} + AB = A \oplus B \end{aligned}$$

i.e. $\boxed{A \oplus B = A \oplus B}$

Now consider

$$\begin{aligned} A \oplus B \oplus C &= [A \oplus B] \oplus C \\ &= (\overline{AB} + AB) \oplus C \\ &= \bar{x}\bar{C} + \bar{x}C \quad (\text{let } x = \overline{AB} + AB) \\ &= x\bar{C} + (\overline{AB} + AB)C \\ &= (\overline{AB} + AB)\bar{C} + (\overline{AB} + AB)C \\ &= (A\bar{B} + \bar{A}B)\bar{C} + (\bar{A}\bar{B} + AB)C \end{aligned}$$

$$A \oplus B \oplus C = A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$$

$$\begin{array}{cccc} & & & \\ & = & A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC \\ & 100 & 010 & 001 \\ M_4 & M_2 & M_1 & M_7 \end{array}$$



$$\therefore A \oplus B \oplus C = \sum m (1, 2, 4, 7)$$

Now consider

$$\begin{aligned}
 A \odot B \odot C &= [A \odot B] \odot C \\
 &= \overline{A \odot B} \bar{C} + (A \odot B) C \\
 &\Rightarrow (\cancel{AB} + \cancel{AB}) C + \cancel{\bar{A} \bar{B}} \\
 &= (A \oplus B) \bar{C} + (A \odot B) C \\
 &= (\bar{A} B + A \bar{B}) \bar{C} + (\bar{A} \bar{B} + A B) C \\
 &= \bar{A} B \bar{C} + A \bar{B} \bar{C} + \bar{A} \bar{B} C + A B C \\
 &= A \bar{B} \bar{C} + \bar{A} B \bar{C} + \bar{A} \bar{B} C + A B C
 \end{aligned}$$

$$\boxed{A \odot B \odot C = A \oplus B \oplus C}$$

Note:

$$\rightarrow \overline{A \oplus B} = A \odot B$$

$$\rightarrow A \oplus B \oplus C = A \odot B \odot C$$

$$\rightarrow \overline{A \oplus B \oplus C \oplus D} = A \odot B \odot C \odot D$$

$$\because x_1 \oplus x_2 \oplus x_3 \oplus \dots \oplus x_n = \begin{cases} x_1 \odot x_2 \odot x_3 \dots \odot x_n, & \text{if } n \text{ is even} \\ x_1 \odot x_2 \odot x_3 \odot \dots \odot x_n, & \text{if } n \text{ is odd} \end{cases}$$

Universal logic gates

\rightarrow NAND, NOR are called universal logic gates, cuz using either of these we can design any boolean function.

All logic gates using NAND, NOR:

(i) NOT:

using NAND




using NOR



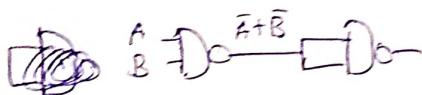(ii) AND:


NAND:

$$\begin{aligned} \text{Req: } AB &= \overline{AB} \\ &= (\overline{A} + \overline{B}) \end{aligned}$$



NOR
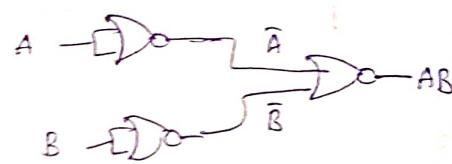
$$\begin{aligned} AB &= \overline{(A+B)} \\ AB &= \overline{\overline{A} \cdot \overline{B}} \end{aligned}$$




(iii) OR:

NAND

Req: $A+B$

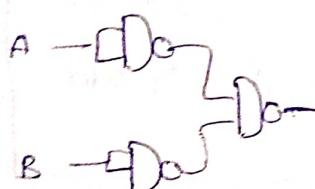avail: $\overline{AB} = \overline{A} + \overline{B}$




NOR

Req: $A+B$


avail: $\overline{A+B} = \overline{\overline{A} \cdot \overline{B}}$



(iv) NAND with NOR:

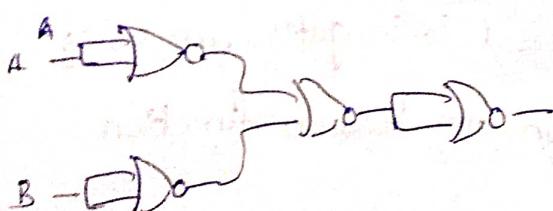


(v) NOR with NAND:

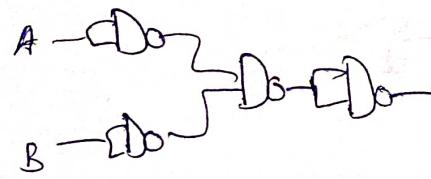


(vi) Ex-OR

using NAND

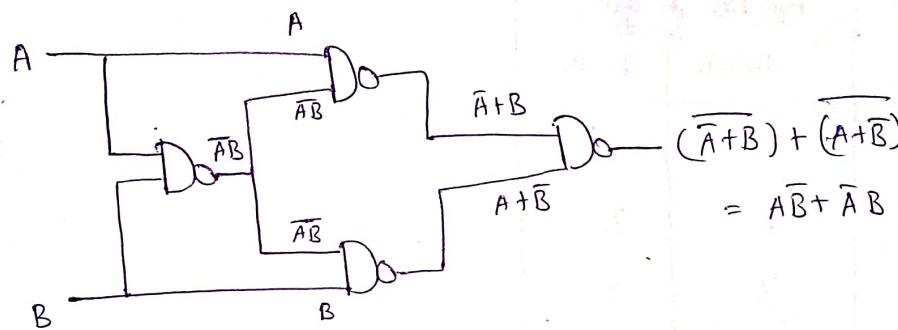


using NOR:

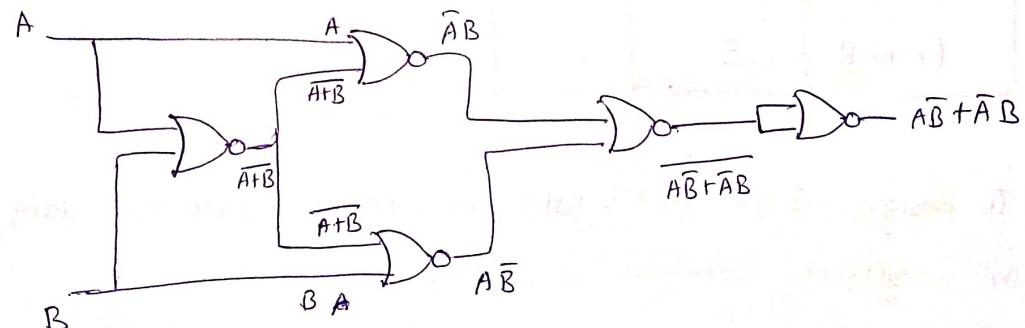


(vii) Ex-NOR

NAND

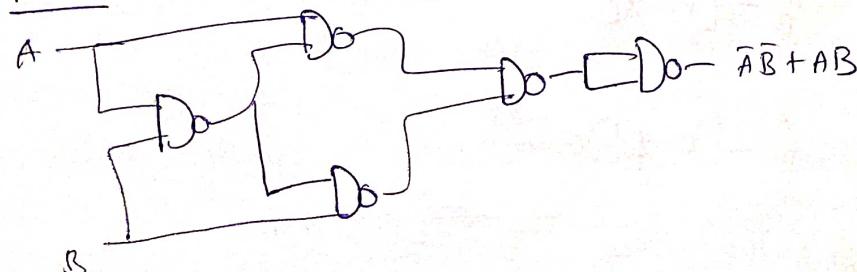

NOR :

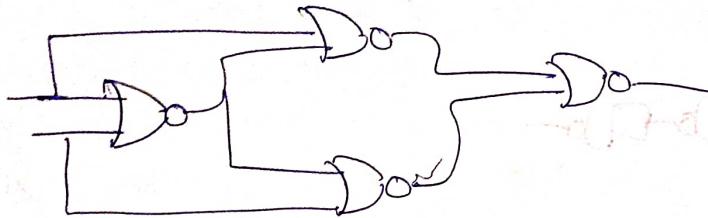

The below table shows min no of NAND & NOR gates req for implementing various gates

gate	min No of gates	
	NAND	NOR
NOT	1	1
AND	2	3
OR	3	2
NAND	1	4
NOR	4	1
Ex-OR	4	5
Ex-NOR	5	4


* Q23 To design 3 i/p NAND gate, min no of 2 i/p nand gate required?

Sol:

$$\text{req: } \overline{ABC} = \overline{\overline{A} + \overline{B} + \overline{C}}$$


$$= \overline{AB} + \overline{C}$$
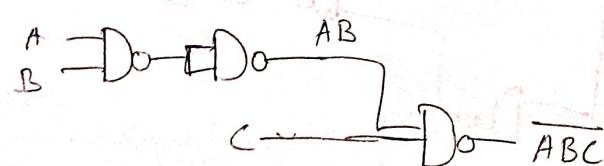
$$\begin{matrix} A \\ B \end{matrix} \Rightarrow \text{Do } \overline{AB}$$



∴ 3

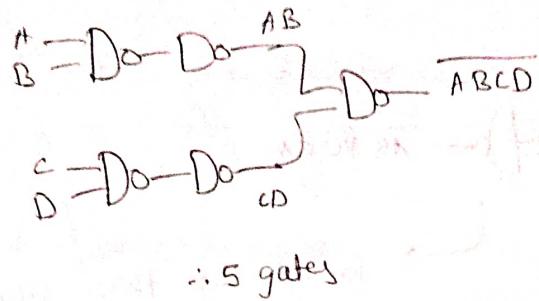Q4 To design 4 i/p min no of 2 i/p NAND gate



Note:

To design "n" i/p NAND gate min no of ~~1 i/p~~ 2 i/p nand gates required is 2^{n-3}

Note:

To design "n" i/p NOR gate min no of 2 i/p NOR gates required is 2^{n-3}

Design any logic function using universal gates

NAND:

→ To design with NAND the given function should be in SOP form.

Procedure:

i. Min no of NAND gates req to implement


$$f = AB + BC + CA$$

$$f = \overline{f} = \overline{AB + BC + CA}$$

~~$$f = \overline{AB} \cdot \overline{BC} \cdot \overline{CA}$$~~

$$f = \overline{AB} \cdot \overline{BC} \cdot \overline{CA}$$
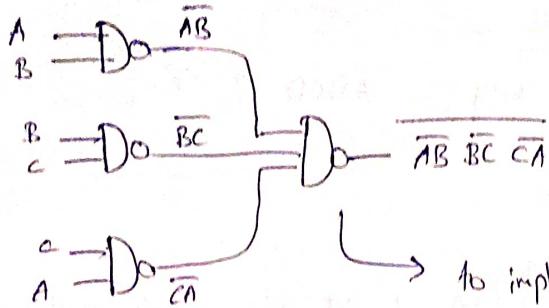
$$f = \overline{\overline{AB} \overline{BC} \overline{CA}}$$



To implement this 3-input NAND gate we need 3 2-input NAND gates.


∴ Min no of NAND gates req to implement given function is 6 NAND gates.

Eg: How many min no of 2-input NAND gates are req to design

$$\text{To implement } f = A + \overline{B}C$$

Sol:
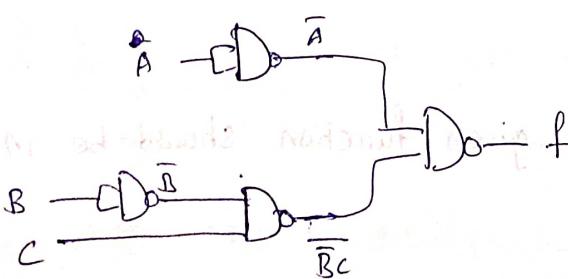
$$f = \overline{\overline{A} + \overline{B}C}$$



NOR:

To design with NOR, the given function should be in POS form.

Eg: Find min no of NOR gates req to design $f = A + BC$

Sol:

$$f = A + BC \text{ is in SOP form}$$

2 NOR gates

each

NOR:

→ To design with NOR gate, the function must be in POS form

$$\cancel{f = A + BC}$$

Ex: Find min no of NOR gates req for $f = A + BC$

Sol:


$$f = A + BC$$

This ~~sop~~ is SOP

$$\therefore f = \overline{(A+B)(A+C)}$$

$$f = \overline{\overline{(A+B)(A+C)}}$$
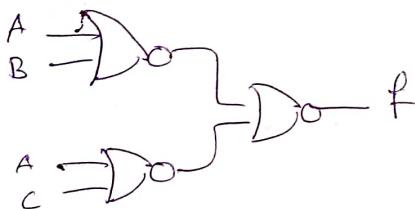
$$f = \overline{\overline{(A+B)}} + \overline{\overline{(A+C)}}$$



∴ 3 2 i/p NOR gates


(Q25) The boolean functions are defined as

$$f_1(A, B, C) = \sum m(0, 1, 3, 5, 6)$$

$$f_2(A, B, C) = \sum m(4, 6, 7)$$

$$f_3(A, B, C) = \sum m(1, 4, 5, 7)$$

to the following circuit.

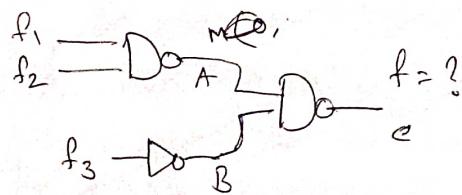

Sol:


$$A = \sum m(0, 1, 2, 3, 4, 5, 7)$$

$$B = \sum m(0, 2, 3, 6)$$

$$\Rightarrow f = \sum m(1, 4, 5, 6, 7)$$

e in pos form

Method 2:

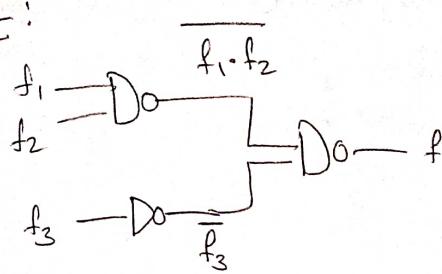

$$f = \overline{f_1 \cdot f_2 \cdot f_3} = \overline{\overline{f_1} \cdot \overline{f_2} + \overline{f_3}}$$

$$= f_1 \cdot \overline{f_2 \cdot f_3}$$

↙
intersection
~~(co)~~

↘ union

$$f_1 \cdot \overline{f_2} = \sum m(6)$$

$$(f_1 \cdot \overline{f_2}) \cup f_3 = \sum m(1, 4, 5, 6, 7)$$

Q) what happens when XORed with itself n times as shown below

$$B \oplus (B \oplus (B \oplus (B \oplus \dots \text{n times}))$$

- a) Complements when "n" is even
- b) complement when "n" is odd
- c) remains unchanged when n is even
- d) remains unchanged when n is odd

SJ:

$$\begin{aligned} 0 \oplus 0 &= 0 \\ 1 \oplus 1 &= 0 \end{aligned}$$

~~ax~~

$$\begin{aligned} 0 \oplus 0 \oplus 0 &= 0 \oplus 0 = 0 \quad \text{bx} \\ 1 \oplus 1 \oplus 1 &= 1 \oplus 0 = 1 \end{aligned}$$

$$0 \oplus 0 \oplus 0 \oplus 0 = 0 \oplus 0 \oplus 0 = 0 \oplus 0 = 0$$

$$1 \oplus 1 \oplus 1 \oplus 1 = 0 \oplus 1 \oplus 1 = 1 \oplus 1 = 0$$

~~∴ from above opt d~~

Here we need to count no of XOR operations
(not variables) ∴ opt C

(Q27) $f(P, Q) = \underbrace{[1 \oplus P]}_{\downarrow} \oplus \underbrace{[P \oplus Q]}_{\downarrow} \oplus \underbrace{[P \oplus Q]}_{\downarrow} \oplus \underbrace{[Q \oplus 0]}_{\downarrow}$

$$\Rightarrow \underline{\overline{P} \oplus 0 \oplus Q}$$

$$\Rightarrow \overline{P} \oplus Q$$


$$= \overline{P} \overline{Q} + \overline{P} Q$$

$$= \overline{P} \overline{Q} + P \overline{Q}$$

$$= P \odot Q$$

02/09/20

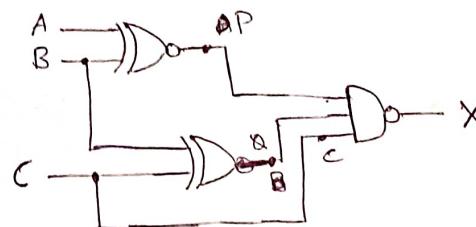(Q28) For the logic circuit shown in figure



The required condition (A, B, C) to make the output $X=0$ is

- a) 1, 1, 1 b) 1, 0, 1 c) 0, 1, 1 d) 0, 0, 1

Sol:

$$P = A \odot B \quad Q = B \oplus C$$

$$X = \overline{P \oplus Q} = \overline{P} \overline{Q}$$

$$= \overline{P} + \overline{Q} + \overline{C}$$

$$= (A \oplus B) + (B \odot C) + \overline{C}$$


$$X=0 \Rightarrow \textcircled{2}$$

$$\Rightarrow A \oplus B = 0 \quad \text{and} \quad B \odot C = 0 \quad \text{and} \quad \overline{C} = 0$$

$$A \oplus B = 0 \quad \leftarrow \quad B \oplus 1 = 0 \quad \leftarrow \quad C = 1$$

$$A = 0$$
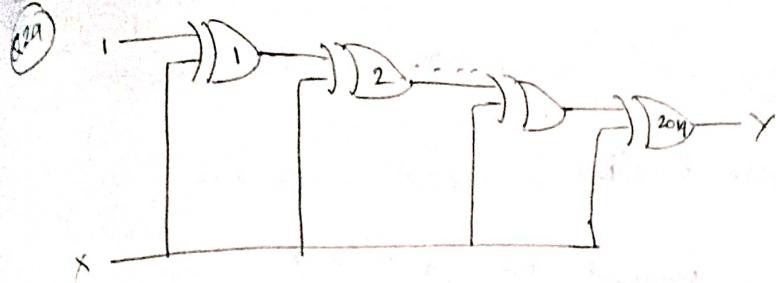
$$\therefore A = 0, B = 0, C = 1 \quad \therefore \text{opt(d)}$$



Then \oplus $Y = ?$

Sol:

$$OP_1 = X \oplus 1 = \bar{X}$$

$$OP_2 = \bar{X} \oplus X = 1$$

$$OP_3 = 1 \oplus X = \bar{X}$$

$$OP_4 = \bar{X} \oplus X = 1$$

$$\therefore OP_{\text{odd}} = \bar{X}, OP_{\text{even}} = 1$$

$$\therefore \underline{\underline{OP}}, \underline{\underline{\text{Ans: } \bar{X}}}$$

(Q3D)

which of the following is self dual

a) $F(A, B, C) = \Sigma m(2, 3, 4, 6)$

b) $F(A, B, C) = \Sigma m(1, 2, 6, 7)$

c) $F(A, B, C) = \Sigma m(0, 4, 5, 7)$

d) $F(A, B, C) = \Sigma m(3, 5, 6, 7)$

~~sol:~~

$$\text{self dual} \Leftrightarrow [x \in m \Rightarrow 2^{n-1-i} \in M]$$

~~op~~ (a)

$$(0, 7) (1, 6) (2, 5) (3, 4)$$

one of these elements is present in self dual function

\therefore op (d)

K-Maps (karnaugh maps)

* used for simplifying boolean function

* It is graphical & systematic method for simplification

* K-maps consists of cells.

n-variable Kmap contains 2^n cells.

* each cell represents a minterm (SSOP) or maxterm (POS)

Method of grouping in K-map:


* 1st group highest possible no of cells

* group of 2 terms is called a pair

* group of 4 terms is called a Quad

* group of 8 terms is called a Octet

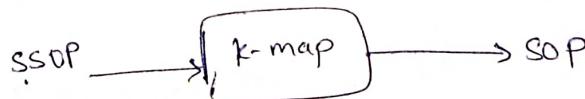K-map Simplified Simplification for SSOP:



3-variable K-map:

* 8 cells

		BC				
		00	01	11	10	
MSB	0	M ₀	M ₁	M ₃	M ₂	
	1	M ₄	M ₅	M ₇	M ₆	

grouped (for min distance)

Alternate way


		AB				
		00	01	11	10	
LSB 4	0	M ₀	M ₂	M ₆	M ₄	
	1	M ₁	M ₃	M ₇	M ₅	

Q: Simplify following Boolean function using K-map.

$$(f(A,B,C) = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C} + ABC)$$


$m_1 \quad m_3 \quad m_6 \quad m_7 \hookrightarrow SSOP$
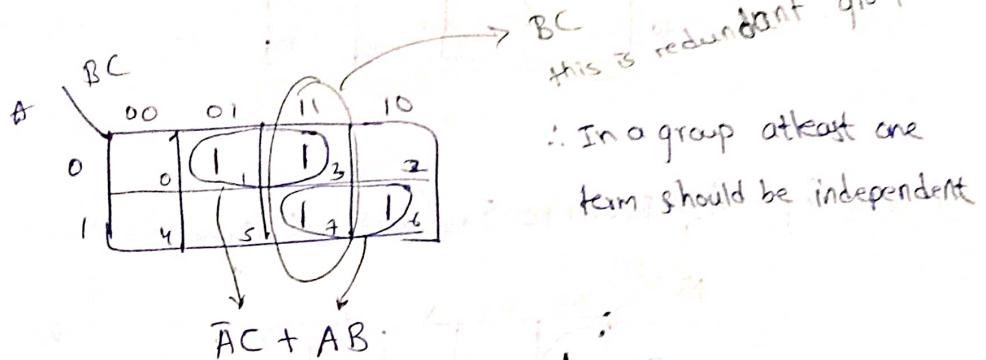
$$\therefore f(A,B,C) = \sum m(1, 3, 6, 7)$$




$$\therefore f(A,B,C) = \bar{A}C + AB$$

Q: $f(A,B,C) = \sum m(1, 2, 5, 6, 7)$

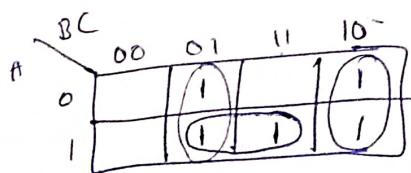

$$\therefore f(A,B,C) = \bar{B}C + AC + BC$$

Method 2:

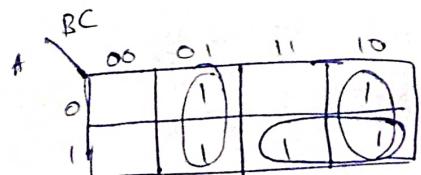

$$f = \bar{B}C + BC + AB$$

Both are simplified
since no A literals are same.

Note:


→ In K-map, simplified expressions need not be unique.

4-variable K-map:

MSB $\leftarrow AB$ LSB $\rightarrow CD$

	00	01	11	10
00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

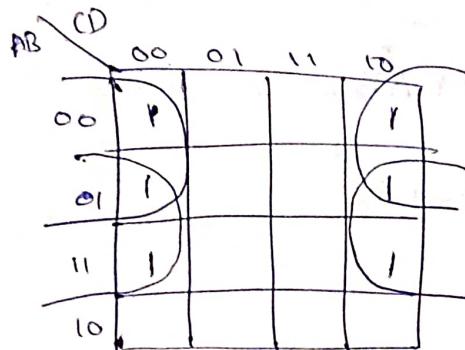Eg: Simplify $f(A, B, C, D) = \sum m(0, 2, 4, 6, 12, 14)$



$$\therefore f(A, B, C, D) = \bar{A}\bar{D} + B\bar{D}$$

(Q3) For the boolean function

$$f(A, B, C, D) = \sum m(1, 5, 6, 7, 11, 12, 13, 15) \quad \text{the minimal SOP is}$$


a) $f = \bar{B}\bar{C}D + \bar{A}BC + BD$

b) $f = \bar{A}\bar{C}D + \bar{A}BC + ACD + ABC\bar{C} + BD$

c) $f = \bar{A}\bar{C}D + \bar{A}BC + ABC\bar{C} + \bar{A}CD + BD$

d) none

Sol:

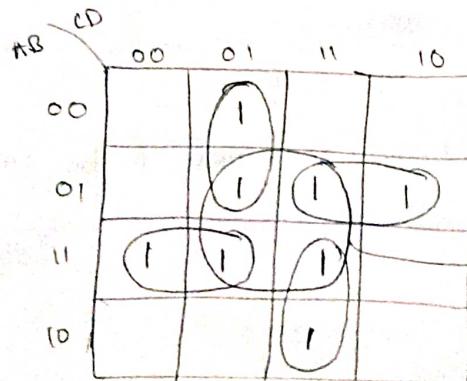

This is not considered,
cuz it has no independent term.

$$\therefore f = A\bar{B}\bar{C} + \bar{A}\bar{C}D + \bar{A}BC + ACD$$

\therefore opt (d)

none

Don't Care:

→ when we don't care about an op/r we consider it don't care.

e.g.: Simplify the following Boolean function

$$f(A,B,C) = \Sigma_m(0,1,3,7) + \Sigma_d(2,4,5)$$


		BC	00	01	11	10
		A	0	1	1	X
0	0	0	1	X	X	1
	1	1	X	X	1	

$$f(A,B,C) = \bar{A} + C$$

* group minterms is compulsory, but grouping of all minterms is not compulsory.

don't cares is not needed.

K-Map Simplification for SPOS:

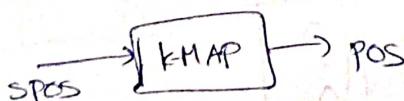

* Each cell indicates Minterm.

$$\text{Q: } f(A,B,C) = \prod_m(0,3,4,7)$$

		BC	00	01	1*	10
		A	0	0	1	2
0	0	0	0	0	0	1
	1	0	1	1	1	0


$B+C$

$$\therefore f(A,B,C) = (B+C)(\bar{B}+\bar{C})$$

Eq: Simplify $f(A, B, C, D) = \pi m(0, 6, 7, 8, 12, 13, 14, 15)$

136

Sol:

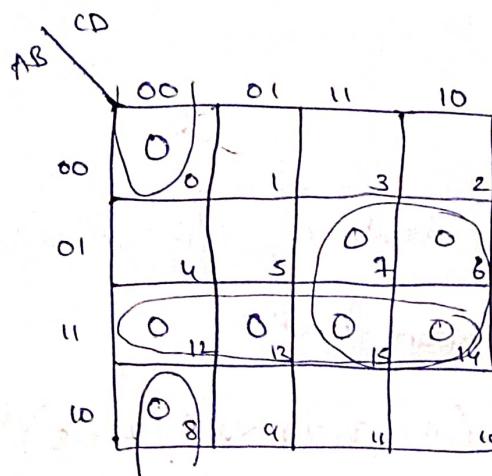


$$f(A, B, C, D) = (B + C + D)(\bar{A} + \bar{B})(\bar{B} + \bar{C})$$

03/09/20

K-Map for SPOS with Don't care:

Eq: Simplify
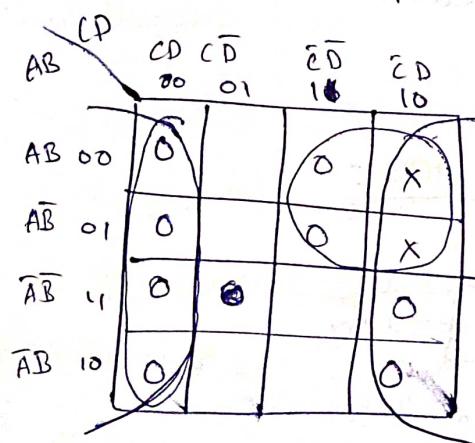
$$f(A, B, C, D) = \pi m(0, 3, 4, 7, 8, 10, 12, 14) + \sum d(2, 6)$$



$$\therefore f(A, B, C, D) = \cancel{A\bar{B}} (A + \bar{C}) \bar{D}$$

Note:

For n variable K-map, group 2^k terms gives a term with $n-k$ no of literals.

Consensus theorem:

$$1 \quad \boxed{xy + \bar{x}z + yz = xy + \bar{x}z}$$

Proof:

$$\begin{aligned} & xy + \bar{x}z + yz \\ &= xy + \bar{x}z + \cancel{(1)}yz \\ &= xy + \bar{x}z + (x + \bar{x})yz \\ &= \underbrace{xy + \bar{x}z}_{(1)} + \underbrace{xyz + \bar{x}yz}_{(2)} \\ &= xy(z+1) + \bar{x}z(y+1) \\ &= xy + \bar{x}z \end{aligned}$$

Special Cases in K-Map:

(Case i):

$$f_1(A, B, C) = \sum m(1, 3, 6, 7)$$

		BC	00	01	11	10
		A	0	1	1	1
		B	0	0	1	1
		C	0	1	1	1

$$f_1 = \bar{A}C + AB$$

(Case ii):

$$f_2(A, B, C) = \pi M(0, 2, 4, 5)$$

		BC	00	01	11	10
		A	0	0	0	0
		B	0	0	0	0
		C	0	0	0	0

$$f_2 = (A+C)(\bar{A}+B) = \underset{1}{\bar{A}} + AB + \bar{A}C + BC$$

$$f_2 = AB + \bar{A}C \quad (\because \text{Consensus theorem})$$

Case (iii)

$$f_3(A, B, C) = \pi M(1, 3, 6, 7)$$

		BC	00	01	11	10
		A	0	0	0	0
			0	0	0	0
0	0	0	0	0	0	0
1	1	0	0	0	0	0

$$f_3 = (A + \bar{C})(\bar{A} + \bar{B})$$

$$\begin{aligned} &= A\bar{A} + A\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C} \\ &= A\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C} \end{aligned}$$

$$f_3 = \bar{A}\bar{B} + \bar{A}\bar{C} \quad (\because \text{consensus theorem})$$

From case(i) & case(ii)

$$f_1 = f_2$$

Consider

$$\begin{aligned} f_1 * f_3 &= (\bar{A}C + AB)(\bar{A}\bar{B} + \bar{A}\bar{C}) \\ &= 0 + 0 + 0 + 0 \\ &= 0 \end{aligned}$$

Product of two function is zero iff they are complements to each other.

$$\therefore f_1 = \overline{f_3}$$

$\therefore \Sigma m(1, 3, 6, 7) = \overline{\pi M(1, 3, 6, 7)}$ (same terms ⇒ complement)
$\Sigma m(1, 3, 6, 7) = \pi M(0, 2, 4, 5)$ (absent terms ⇒ equal)

XOR & XNOR

A B	$A \oplus B$	$A \otimes B$
0 0	0	1
0 1	1	0
1 0	1	0
1 1	0	1

XOR

O/P = 1, if no of 1's is odd

Hence XOR is called odd logic gate.

XNOR

O/P = 1, if no of 1's is even

Hence XNOR is called even logic gate

Note:

1) If XNOR is called equality detector or coincident detector

2) If XOR is called inequality detector or anti-coincident detector

Prime Implicants (PI)

Implicant: It is a set of all adjacent minterms.

i.e., group of all possible combinations of octet, quad, pair etc.


(Here we don't need to follow k-map redundant rules)

Prime implicant:

It is implicant which is not a subset of another implicant.

(no need to follow redundant property)

Case (i)

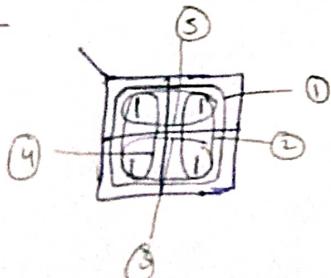

Here ② is subset of ①

③ " " " ①

④ " " " ①

⑤ " " " ①

M is the only prime implicant, but not ② ③ ④ ⑤

→ Prime implicants are classified into 2 types

i) Essential Prime Implicant


ii) Non-essential prime implicant

iii) Selective PI iv) Redundant PI

Essential Prime Implicant:

It is a PI which contains at least one independent minterm from other prime implicants.

Case i):

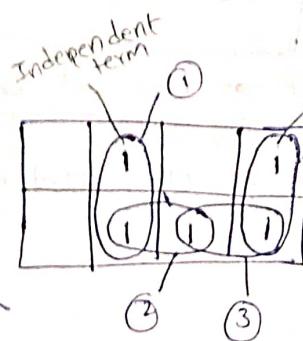


$$\text{PIs} \Rightarrow 1, 2, 3, 4$$

$$\text{EPIs} \Rightarrow 1, 4$$

$$\text{NEPIs} \Rightarrow 2, 3$$

Case iii):

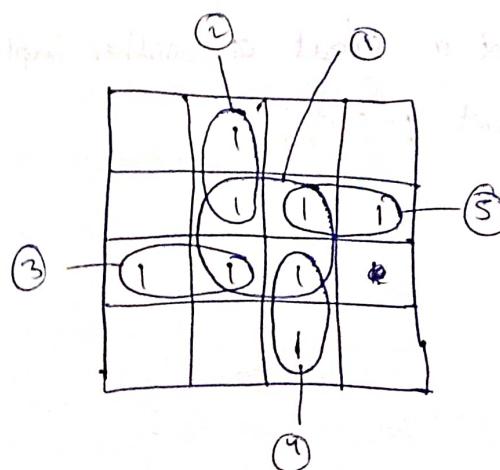


$$\text{PIs} \Rightarrow 1, 2, 3, 4, 5$$

$$\text{EPIs} \Rightarrow 1, 2, 3, 4, 5$$

$$\text{NEPIs} \Rightarrow 1$$

Find no of PI, EPI
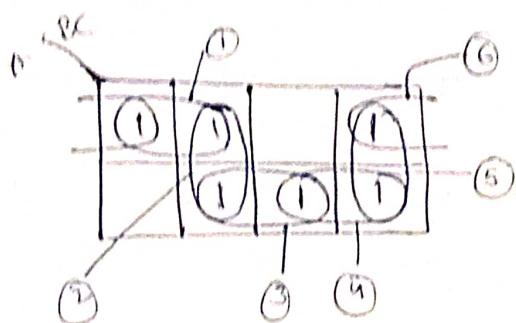
$$f(A, B, C) = \sum m(0, 1, 2, 5, 6, 7)$$




No of PIs = 6

No of EPIS = 0

Find PI, EPI for function


$$f(A, B, C, D) = \sum m(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$$

Sol:

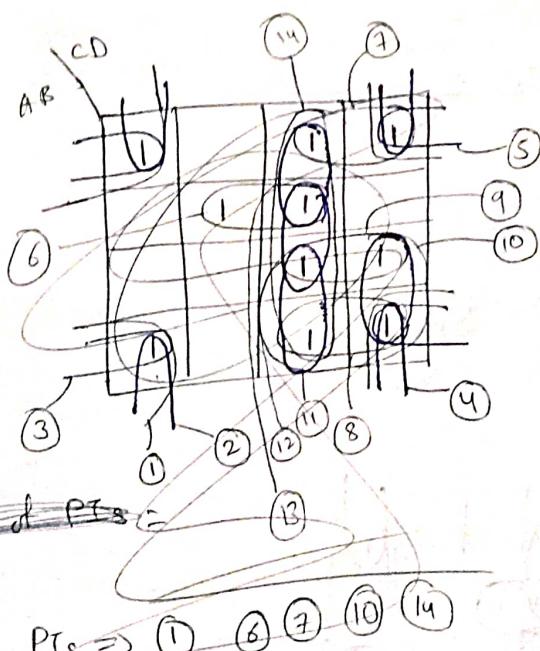

No of PIs

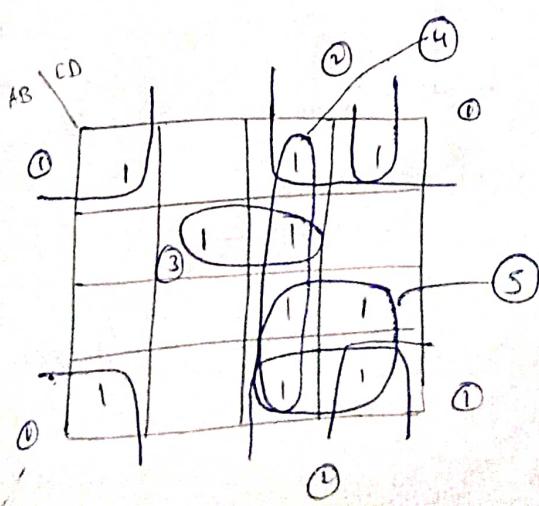PIs $\Rightarrow (0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$




\therefore no of PIs = 5

no of EPIS = 2 (i.e., ④ ⑤)

(Q33) Find no of PIs, EPIs for

$$f(A, B, C, D) = \sum m(6, 7, 8, 9, 13, 15)$$

Sol:

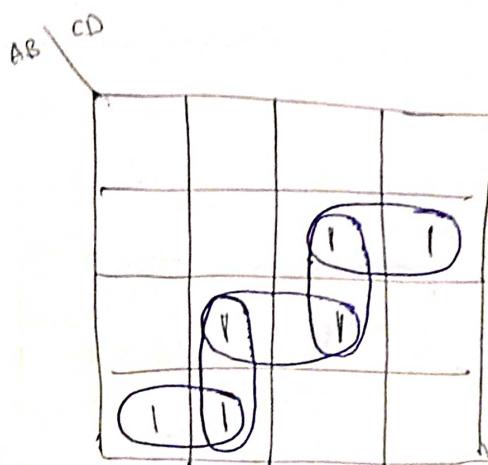

\therefore no of PIs = 5


no of EPIS = 2

(Q34)

Find no of PIs of function

$$f(w, x, y, z) = \sum m(0, 2, 4, 5, 6, 10)$$

Sol:

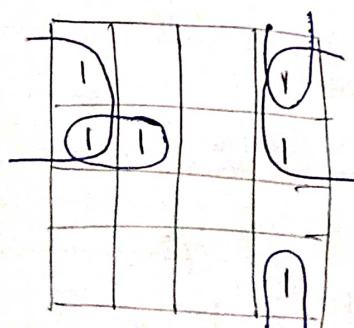

\therefore no of PIs = 3

Combinational Logic Circuits


- The circuit in which present o/p depends on present input but not previous data is called as combinational logic circuit.
- Adders, subtractors, Magnitude comparator, Encoder, Decoder, Multiplexer & Demultiplexers.

04/09/20

Adders & Subtractors

Half Adder (HA):

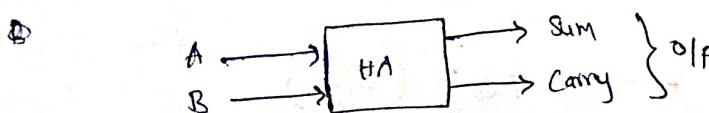
- It is a combinational logic circuit that contains 2 i/p's & 2 o/p's.




truth table

Inputs		O/P	
A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1
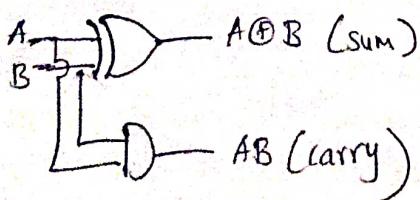
$$\begin{aligned} \text{Sum} &= A \oplus B \\ \text{Carry} &= AB \end{aligned}$$




Half Subtractor (HS)

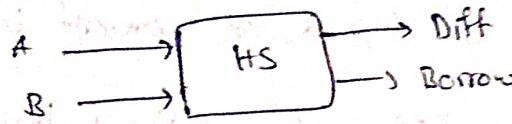

A	B	Diff	Borrow
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$\therefore \text{Difference} = A \oplus B$$

$$\text{Borrow} = \bar{A}B$$

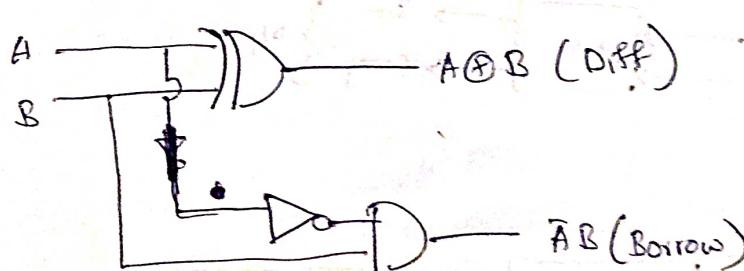

Full Adder:

→ 3 i/p's & 2 o/p's



A	B	C	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

$$FA_{\text{sum}} = \Sigma m (1, 2, 4, 7)$$

$$FA_{\text{carry}} = \Sigma m (3, 5, 6, 7)$$

Sum

	BC	00	01	11	10
A	0	0	1	1	1
B	0	1	1	0	0
C	0	0	0	1	1

$$\begin{aligned} \text{Sum} &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\ &= \bar{A}(\bar{B}C + B\bar{C}) + A(\bar{B}\bar{C} + BC) \\ &= \bar{A}(B \oplus C) + A(B \oplus C) \\ &= \bar{A}(B \oplus C) + A(\overline{B \oplus C}) \end{aligned}$$

$$FA_{\text{sum}} = A \oplus B \oplus C$$



Carry

	BC	00	01	11	10
A	0	0	0	1	1
B	0	1	1	0	0
C	0	0	0	0	1

$$FA_{\text{carry}} = BC + AC + AB$$


$$FA_{\text{carry}} = AB + BC + CA$$

Logic diagram:

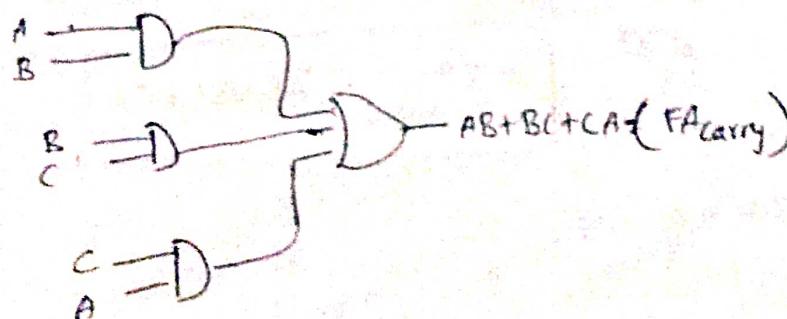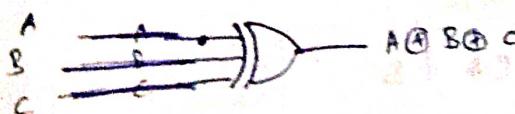

Full Subtractor:

146

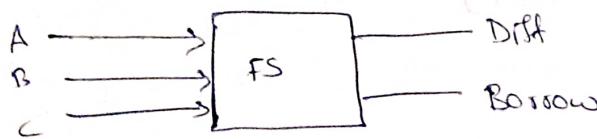



A	B	C	Diff	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$(A-B)-C$$

$$\therefore F_{\text{Diff}} = \sum m(1, 2, 4, 7)$$

$$\therefore F_{\text{Diff}} = A \oplus B \oplus C$$
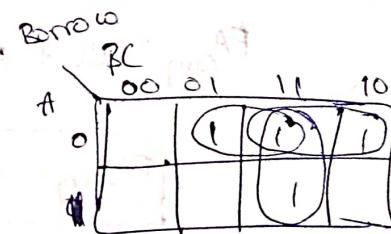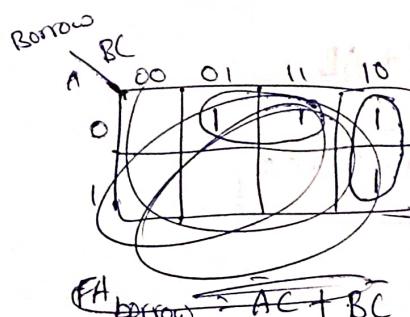
$$F_{\text{Borrow}} = \sum m(1, 2, 3, 7)$$




$$F_{\text{Borrow}} = \bar{A}C + \bar{A}B' + BC$$

~~$$\therefore F_{\text{Borrow}} = \bar{A}B + BC + CA$$~~

logic diagram
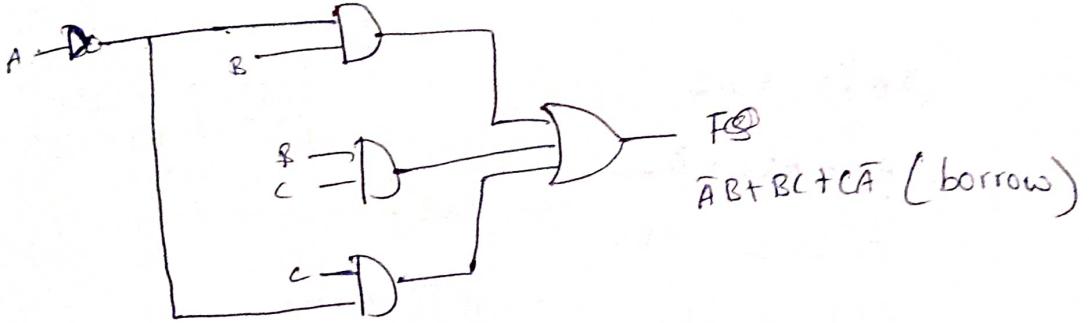
$$\text{A} \oplus \text{B} \oplus \text{C} \quad (\text{diff})$$



Note:

$$\begin{aligned} \text{HA} & \begin{cases} \text{sum: } A \oplus B \\ \text{carry: } AB \end{cases} \end{aligned}$$

$$\begin{aligned} \text{HS} & \begin{cases} \text{diff: } A \oplus B \\ \text{borrow: } \bar{A}B \end{cases} \end{aligned}$$

$$\begin{aligned} \text{FA} & \begin{cases} \text{sum: } A \oplus B \oplus C \\ \text{carry: } AB + BC + CA \end{cases} \end{aligned}$$

$$\begin{aligned} \text{FS} & \begin{cases} \text{diff: } A \oplus B \oplus C \\ \text{borrow: } \bar{A}B + BC + CA \end{cases} \end{aligned}$$

FA using HA:

- (Q5) To design number of half adder, basic gates required to design full adder respectively are _____

Sol:

$$\text{FA}_{\text{sum}}: A \oplus B \oplus C$$


$$\text{HA}_{\text{sum}}: A \oplus B$$

$$\text{FA}_{\text{carry}}: AB + BC + CA$$

$$\text{HA}_{\text{carry}}: AB$$


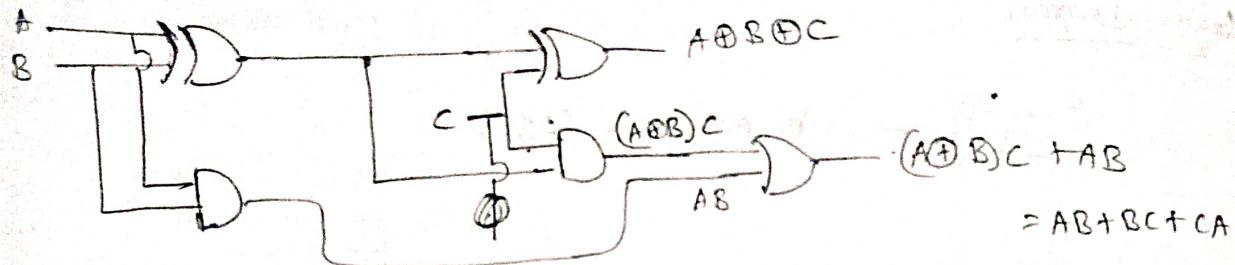
$$\begin{aligned} & \# \text{A} \oplus \text{B} \oplus \text{C} \\ & (A \oplus B) \oplus C \\ & = \bar{A}BC + A\bar{B}C \end{aligned}$$



$$(A \oplus B)C + AB$$

$$= AB + A\bar{B}C + \bar{A}BC$$

$$A(B + \bar{B}C) + \bar{A}BC$$

$$A(B + C) + \bar{A}BC$$

$$AB + \cancel{AC} + \bar{A}BC$$

$$AC\cancel{B} + B(A + \bar{A}C)$$

$$AC\cancel{B} + B(A + C)$$


~~$\cancel{B} + AB$~~

$$= AC + AB + BC$$

$$\therefore (A \oplus B)C + AB = AB + BC + AC$$

\therefore 2 HA and 1 basic gate (OR)

Full Subtractor using half subtractor

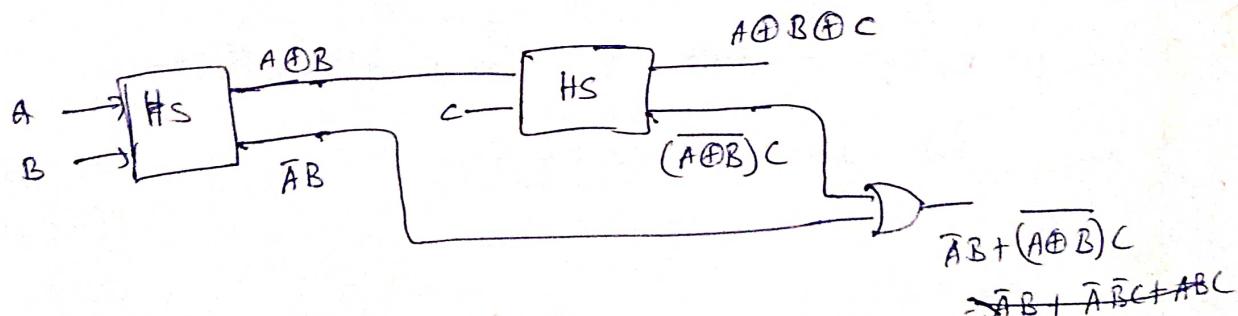

$$\bar{A}B + (\bar{A}\bar{B} + B\bar{A})C$$

$$= \bar{A}B + \bar{A}\bar{B}C + ABC$$

$$= \bar{A}B + \bar{A}C + ABC$$

$$= \bar{A}B + C(\bar{A} + AB)$$

$$= \bar{A}B + BC + \bar{A}C$$


\therefore For FS, we need

2 HS + 1 OR

~~$\bar{A}B + \bar{A}\bar{B}C + ABC$~~


Design of Adders, Subtractors using universal logic gates

HA using NAND

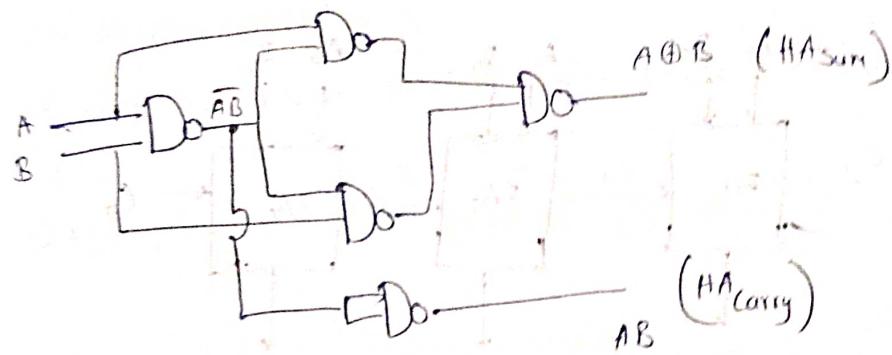

→ For HA minimum NAND gates required = 5

FA using NAND

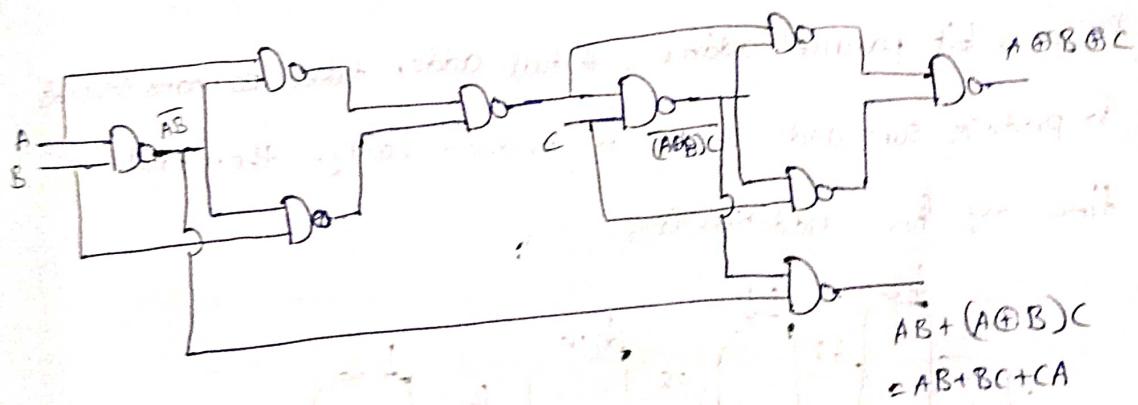

∴ 9 NAND gates for FA.

Note:


	NAND	NOR
HA	5	5
HS	5	5
FA	9	9
FS	9	9

15/10/20

150

Binary Adder or Parallel Adder:

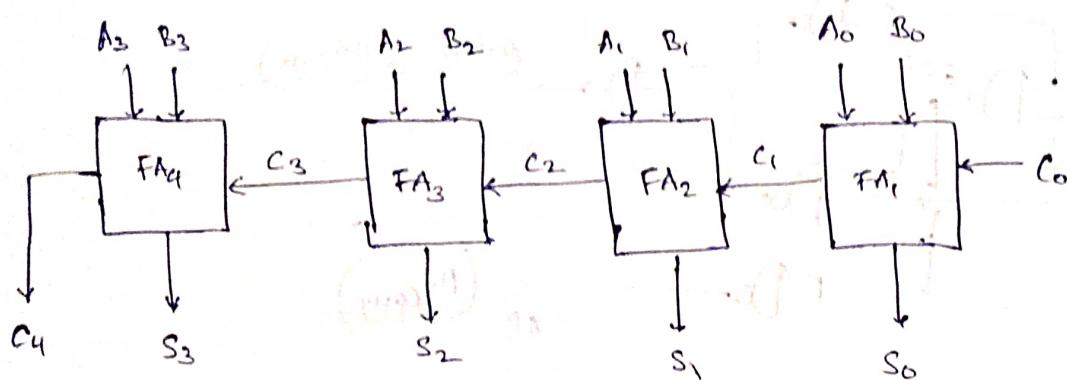Consider 4 bit parallel adder as shown below




- (Q36) To design 17 bit parallel adder, find min no of HA, basic gates req.

Ans: 33 HA, 16 OR gates

$\therefore 33, 16$

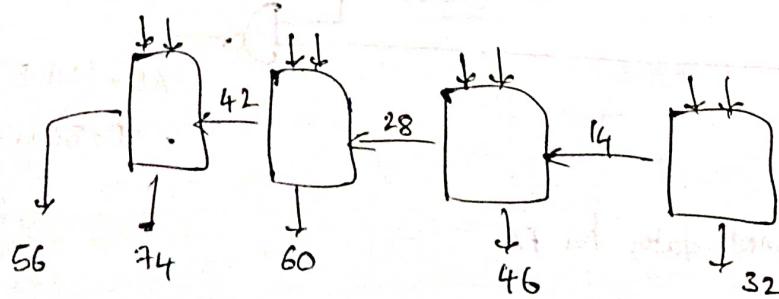- (Q37) In a 4 bit parallel adder, a full adder takes 32 nano seconds to produce sum and 14 ns to produce carry. Then total time req for addition is



$\therefore 74 \text{ ns}$

Note:


For an n-bit parallel adder, time req to produce sum

$$= (n-1)t_{\text{carry}} + \max(t_{\text{carry}}, t_{\text{sum}})$$

disadvantage:

- In binary adder carry at any stage depends on previous carries. Hence it takes more time for addition.
- It is slowest adder.
- we can overcome above problem using carry lookahead adder.

Carry Lookahead Adder (CLA)

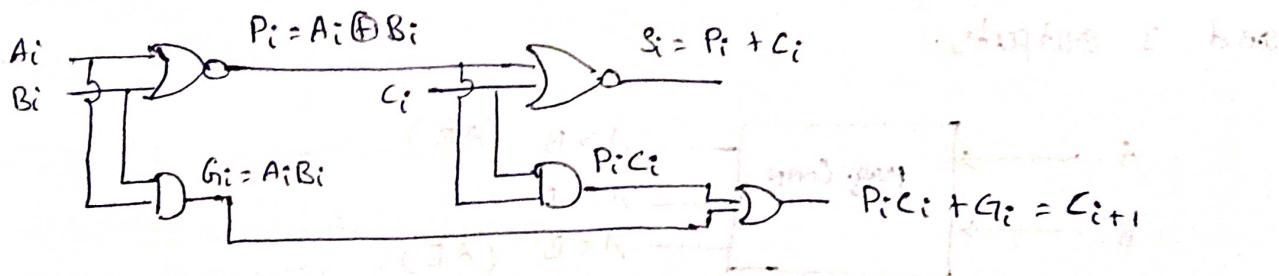

$$i=0 \Rightarrow C_{i+1} = G_i + P_i C_i$$

$P_i \rightarrow$ Carry Propagate

$$i=0 \Rightarrow C_1 = G_0 + P_0 C_0$$

$G_i \rightarrow$ Carry Generate.

$$i=1 \Rightarrow C_2 = G_1 + P_1 C_1$$

$$= G_1 + P_1 (G_0 + P_0 C_0)$$

$$= G_1 + P_1 G_0 + P_1 P_0 C_0$$

$$i=2 \Rightarrow C_3 = G_2 + P_2 C_2$$

$$= G_2 + P_2 (G_1 + P_1 G_0 + P_1 P_0 C_0)$$

$$= G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

$$i=3 \Rightarrow C_4 = G_3 + P_3 C_3$$

$$= G_3 + P_3 (G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0)$$

$$C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$$

- At any stage carry look ahead adder is independent of previous carries. Hence CLA is faster than binary adder.


→ But, internal circuit of CLA consists of AND gates, OR gates etc.
for 'n' bit CLA,

$$\left. \begin{array}{l} \text{no of AND gates} = \frac{n(n+1)}{2} \\ \text{no of OR gates} = n \end{array} \right\} \begin{array}{l} \text{This is valid when all} \\ \text{ctrl p. are available} \\ \text{and AND, OR can take} \\ \text{any no of inputs} \end{array}$$

Magnitude Comparator:

(n) digit binary num.

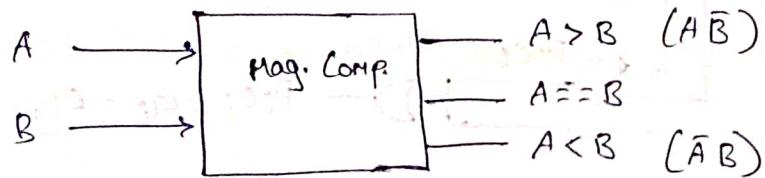It is a combinational circuit which consists of 2 inputs and 3 outputs.



→ In n bit mag. Comp. no of combinations = $2^n \cdot 2^n = 2^{2n}$

→ In n bit mag. Comp. no of i/p for which

* $A = B$ is 2^n

* $A > B$ is $\frac{2^{2n} - 2^n}{2}$


* $A < B$ is $\frac{2^{2n} - 2^n}{2}$

Full Adder:


Encoders & Decoders

Encoder:

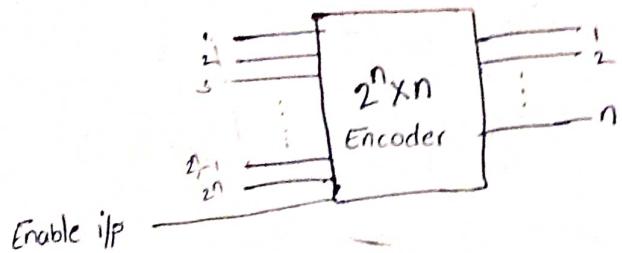It is a combinational logic circuit, which consists of 2^n inputs and n outputs.



Eg.:

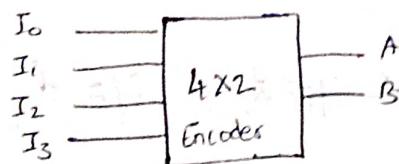

- Encoder is used to reduce no of data lines, in the O/P.
- It converts decimal or (any number system), to binary.

Design 4x2 encoder

I/P				O/P	
I ₃	I ₂	I ₁	I ₀	Y ₁	Y ₀
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

In encoder at a time one i/p should be active.

Disadvantage:

- If more than one i/p are active the encoder provides invalid output.
- we can overcome above problem using priority encoder.

4x2 Priority Encoder:


I/P				O/P	
I_3	I_2	I_1	I_0	Y_1	Y_0
0	0	0	1	0	0
0	0	1	X	0	1
0	1	X	X	1	0
1	X	X	X	1	1

I_k has higher priority than
 $I_j \& j < k$

Decoder:

→ It is inverse of encoder.

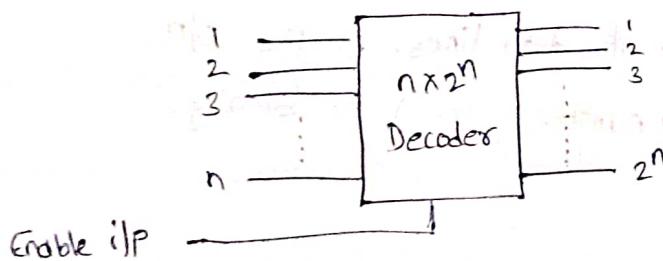→ Defn: Decoder is a CLC with ~~2^n input~~ 'n' i/p & 2^n o/p.



enable i/p:

Enable i/p is used to control the operation of encoder or decoder.

Types of enable i/p:

i) Active high enable i/p:

ii) Active low enable i/p:

154

Decoder converts binary to decimal (or any other number system)

priority that

Based on O/P nature, there are 2 types of decoders

i) Active high O/P decoder:

If active high O/P decoder is disabled all O/P bits are forced to 0.

ii) Active low O/P decoder:

If active low O/P decoder is disabled, then all O/P bits are forced to 1.

f 2^n O/P.

Design 2×4 Decoder:

i) Active high O/P decoder with active high enable I/P:

ii) Active high O/P decode with active low enable I/P

iii) Active low O/P decoder with active high enable I/P

iv) Active low O/P decoder with active low enable I/P

Active high O/P decoder with active high EI:

encoder


I/P			O/P			
EI	A	B	Y_0	Y_1	Y_2	Y_3
0	x	x	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

$$Y_0 = E \bar{A} \bar{B}$$

$$Y_1 = E \bar{A} B$$


$$Y_2 = E A \bar{B}$$

$$Y_3 = E A B$$

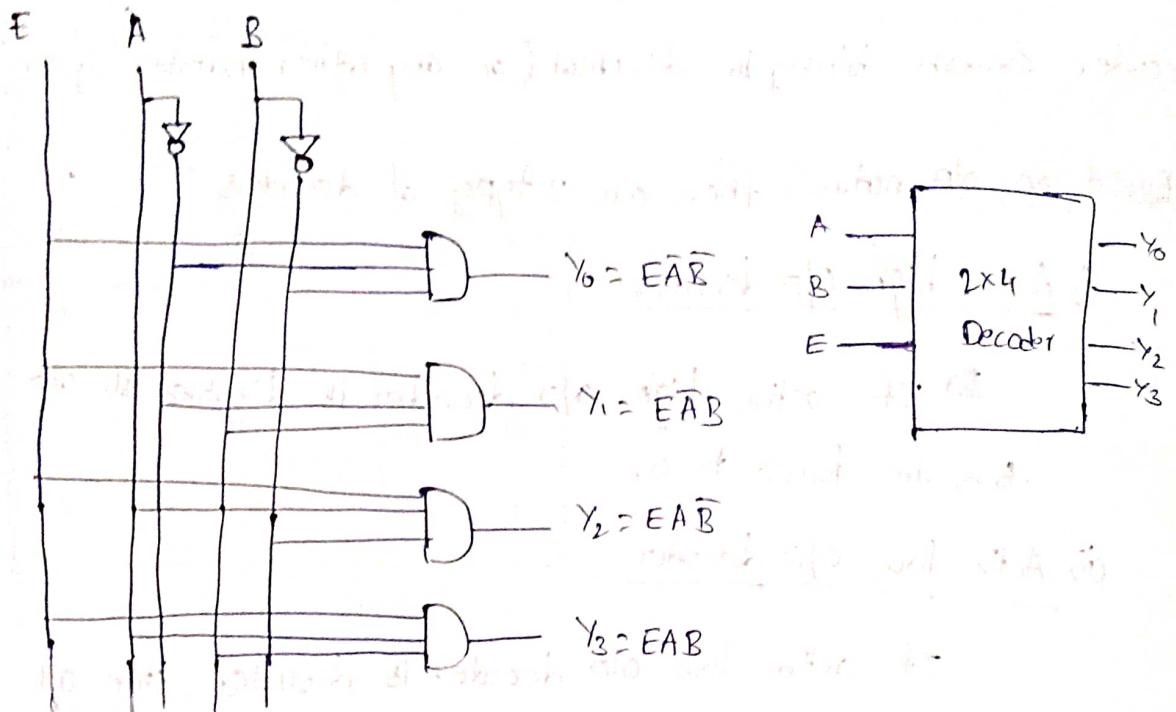

Active high DIP decoder with active low EI :



I/P			O/P			
E	A	B	Y ₀	Y ₁	Y ₂	Y ₃
1	X	X	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1

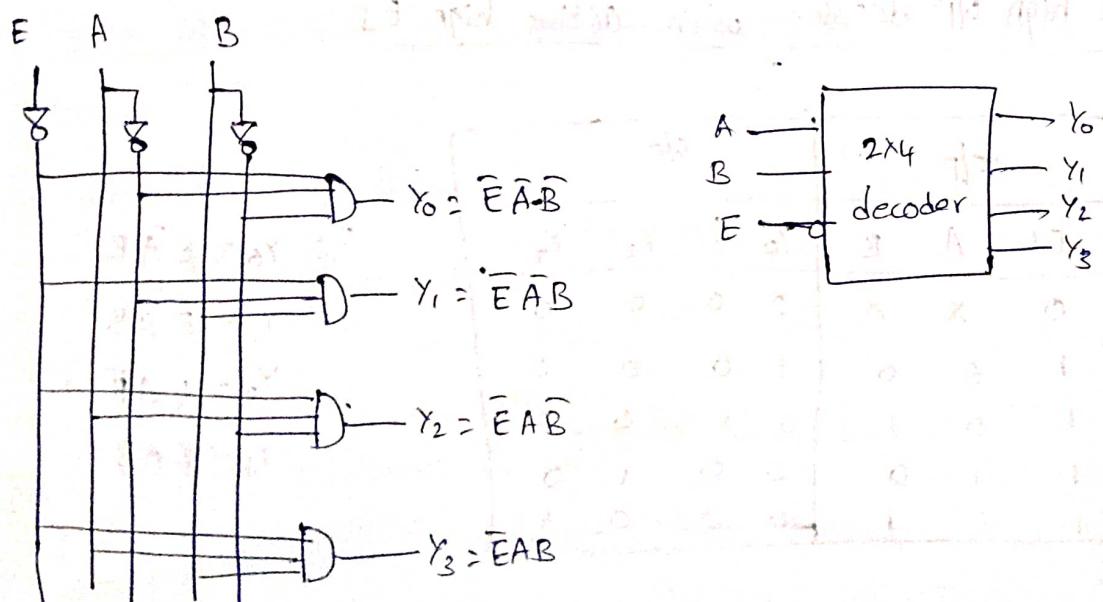

Active low O/P decoder with active high EI:

I/P			O/P			
E	A	B	Y ₀	Y ₁	Y ₂	Y ₃
0	X	X	0	0	1	1
1	0	0	0	1	1	1
1	0	1	1	0	1	1
1	1	0	1	1	0	1
1	1	1	1	1	1	0



E A B

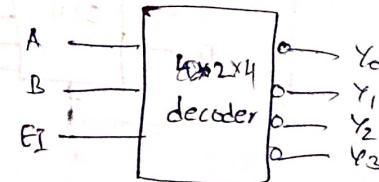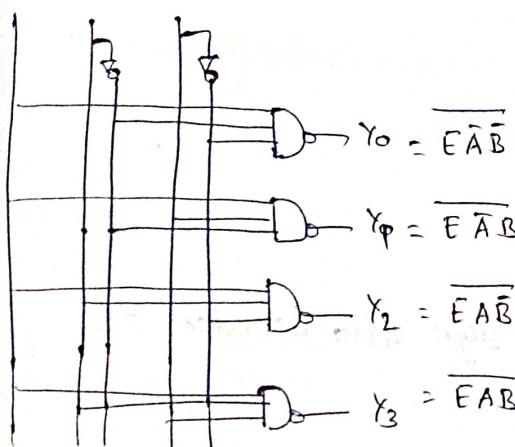

Active low O/P decoder with active active low EI


I/P			O/P			
E	A	B	Y ₀	Y ₁	Y ₂	Y ₃
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0

E A B

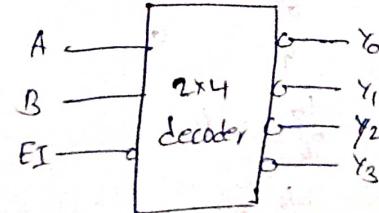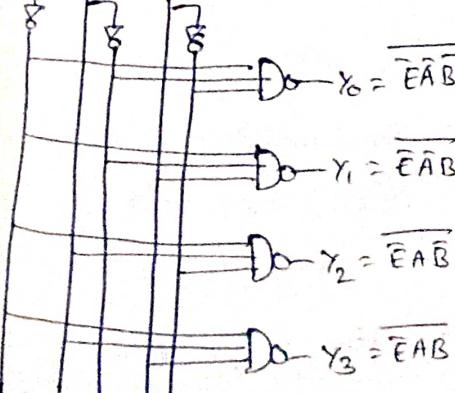

Design 4×16 decoder using 2×4 decoders.

18

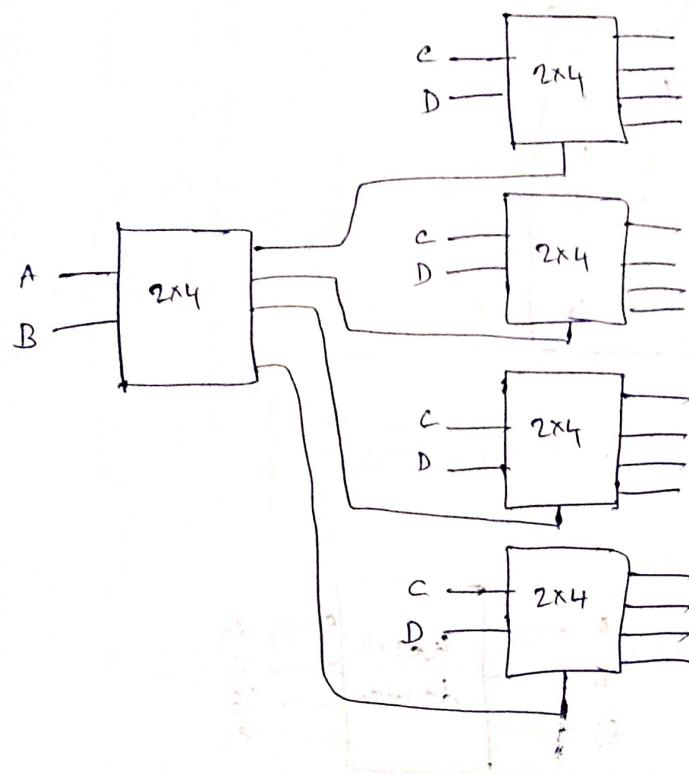

A	B	C	D
0	0	0	0
0	1	1	0
1	0	1	1
1	1	0	1
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

\therefore no of 2×4 decoder req. to design 4×16 decoder = 5.

Shortcut :

→ Recursively divide no of output lines req with given no of output lines until we obtain 1.

Eg: Find no of 2×4 decoders req to design 1024×1024

$$\Rightarrow \frac{1024}{4} = 256$$

$$\frac{256}{4} = 64$$

$$\frac{64}{4} = 16$$

$$\frac{16}{4} = 4$$

$$\frac{4}{4} = 1$$

\therefore no of 2×4 decoders req = $1 + 4 + 16 + 64 + 256$